

The Simulation of Switched Capacitor Circuits

Using Spice AC Simulation (Version 2)

Christian Enz (christian.enz@epfl.ch)

09.08.2026

This notebook presents how to simulate switched-capacitor (SC) circuits and particularly filters in the frequency domain with AC simulation using Spice simulators such as LTSpice or ngspice.

Table of contents

1	Introduction	4
2	Simulation of SC circuits with Spice	5
2.1	Continuous-time model of a switched-capacitor	5
2.2	LTSpice SC components library	6
2.3	Approximation of time delay in ngspice	8
3	Example 1: First-order passive low-pass filter	11
3.1	Simulations	13
3.1.1	LTSpice	13
3.1.2	ngspice	13
4	Example 2: First-order active low-pass filter	17
4.1	Simulations	18
4.1.1	LTSpice	18
4.1.2	ngspice	20
5	Example 3: Second-order active low-pass filter	22
5.1	Simulations	23
5.1.1	LTSpice	23
5.1.2	ngspice	26
6	Example 4: Third-order active low-pass filter	27
6.1	Simulations	29
6.1.1	LTSpice	29
6.1.2	ngspice	29
7	Example 5: Third-order elliptic low-pass filter	32
7.1	Simulations	34
7.1.1	LTSpice	34
7.1.2	ngspice	35
8	Non-ideal effects	39
8.1	Switches	39
8.2	OPAMP or OTA	39
9	Conclusion	41
	References	42

1 Introduction

This notebook presents how to simulate switched-capacitor (SC) circuits and particularly filters in the frequency domain with AC simulation using Spice simulator such as LTSpice [1] or ngspice [2]. The following theory is based on [3] [4]. Because SC circuits are not linear time invariant (non-LTI), they normally cannot be simulated in AC with a conventional Spice circuit simulator. However, we can use the special library that was developed by C. Enz for the AC simulation of SC circuit with two 50% duty-cycle non-overlapping clocks. This library basically simulates the circuits in phase Φ_1 and Φ_2 concurrently and then insures the charge conservation between the two circuits of phase Φ_1 and phase Φ_2 .

i Note

The library for LTSpice includes symbols that can be used for schematic capture of SC circuits making the simulations of SC circuits straightforward.

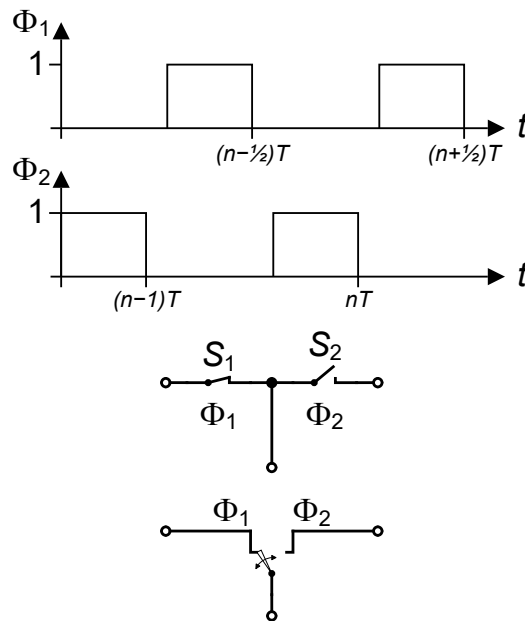


Figure 1.1: Two switches controlled by two non-overlapping phases and the equivalent toggle switch.

We will focus on two phases SC circuits which operate with two non-overlapping phases Φ_1 and Φ_2 as shown in Figure 1.1. Phase Φ_1 controls switch S_1 , whereas phase Φ_2 controls switch S_2 . Switch S_1 is closed when phase Φ_1 is high and switch S_2 is closed when phase Φ_2 is high. Since phase Φ_1 and Φ_2 are non-overlapping, it means that switches S_1 and S_2 are never closed at the same time avoiding any short-circuit between the input and output. This means that they can be replaced by a toggle switch as shown in Figure 1.1.

We start describing the technique used for AC simulation in Spice and illustrate it with the design of various filters.

2 Simulation of SC circuits with Spice

2.1 Continuous-time model of a switched-capacitor

SC circuits are linear circuits but they are not time-invariant (LTI) because the circuit during one phase (say phase Φ_1) is not the same than the circuit in other phases (say Φ_2 for a two phases system). However, the circuit in each phase is LTI and can be simulated with Spice. The basic idea for a two non-overlapping phases SC circuit is to enter the netlist corresponding to each phase Φ_1 and Φ_2 and couple them with a special SC component that ensures the charge conservation between the two phases.

Let's consider a SC as shown in the left figure of Figure 2.1 with the phases Φ_1 and Φ_2 shown on top where $T = 1/f_s$ is the sampling period and D the duty cycle which is usually equal to $1/2$.

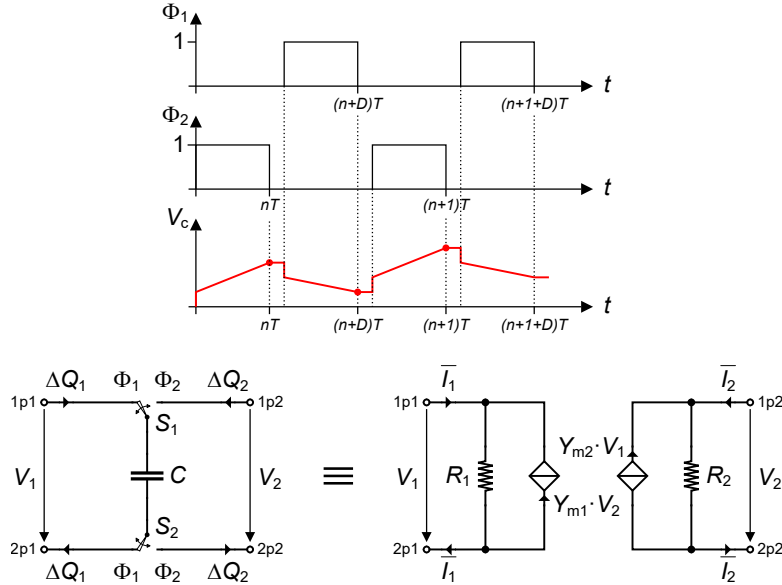


Figure 2.1: Switched-capacitor C and its equivalent continuous-time equivalent.

We can write the following charge conservation equations for capacitor C

$$\Delta Q_1((n+D)T) = C \cdot [V_1((n+D)T^-) - V_2(nT^-)], \quad (2.1)$$

$$\Delta Q_2((n+1)T) = C \cdot [V_2((n+1)T^-) - V_1((n+D)T^-)], \quad (2.2)$$

where ΔQ_1 corresponds to the change of charge on capacitor C between the end of phase Φ_1 and Φ_2 and ΔQ_2 is the change of charge on capacitor C between the end of phase Φ_2 and Φ_1 . The above charge equations can be replaced by the average currents $\bar{I}_1$ and $\bar{I}_2$

$$\bar{I}_1 = \frac{C}{T} \cdot [V_1((n+D)T^-) - V_2(nT^-)], \quad (2.3)$$

$$\bar{I}_2 = \frac{C}{T} \cdot [V_2((n+1)T^-) - V_1((n+D)T^-)], \quad (2.4)$$

where the average currents $\overline{I}_1$ and $\overline{I}_2$ are defined by

$$\overline{I}_1((n+D)T) = \frac{1}{T} \cdot \int_{nT}^{(n+D)T} i_c(t) dt = \frac{\Delta Q_1((n+D)T)}{T}, \quad (2.5)$$

$$\overline{I}_2((n+1)T) = \frac{1}{T} \cdot \int_{(n+D)T}^{(n+1)T} i_c(t) dt = \frac{\Delta Q_2((n+1)T)}{T}. \quad (2.6)$$

The currents can then be written in the z -domain as

$$\overline{I}_1 = \frac{C}{T} \cdot [V_1(z) - z^{-D} V_2(z)], \quad (2.7)$$

$$\overline{I}_2 = \frac{C}{T} \cdot [V_2(z) - z^{-(1-D)} V_1(z)]. \quad (2.8)$$

The above equations can be modelled by the equivalent continuous-time circuit shown on the bottom right of Figure 2.1 where

$$R_1 = R_2 = R_{eq} = \frac{T}{C} \quad (2.9)$$

and

$$Y_{m1} = G_{meq} \cdot e^{-sDT}, \quad (2.10)$$

$$Y_{m2} = G_{meq} \cdot e^{-s(1-D)T}, \quad (2.11)$$

with

$$G_{meq} = \frac{1}{R_{eq}}. \quad (2.12)$$

The continuous-time equivalent is easy to implement in Spice using the Laplace instruction for implementing the time delays e^{-sDT} and $e^{-s(1-D)T}$. This Laplace operator is available in LTSpice but unfortunately it is not available in ngspice. However, we can replace it by using the XSpice s_xfer element which allows implementing a transfer function given by a rational function in s provided the order of the denominator is equal or larger than the order of the numerator.

2.2 LTSpice SC components library

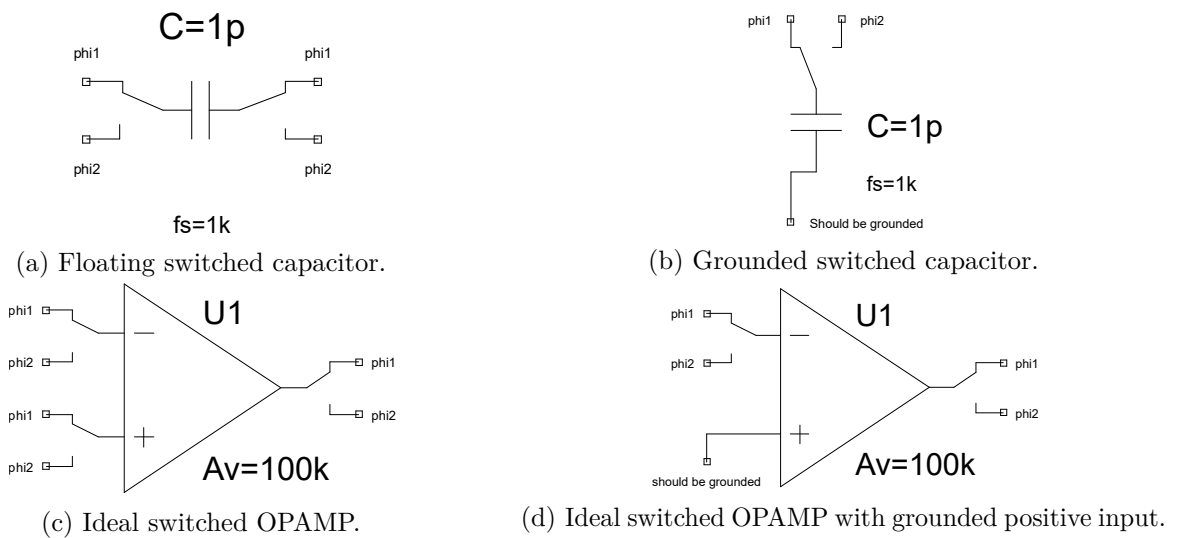


Figure 2.2: LTSpice SC component library.

I designed a LTSpice library including four components which symbols are illustrated in Figure 2.2. The floating switched capacitor of Figure 2.2a calls a subcircuit in my LTSpice analog.lib library having the following code:

```

* Switched capacitor
* -----
.subckt SC 1p1 2p1 1p2 2p2
* Parameters:
* C=1p
* fs=1k
* D=0.5
.param Req={1/(fs*C)} Gmeq={1/Req}
R1 1p1 2p1 {Req}
G1 2p1 1p1 1p2 2p2 Laplace=Gmeq*exp(-s*D/fs)
R2 1p2 2p2 {Req}
G2 2p2 1p2 1p1 2p1 Laplace=Gmeq*exp(-s*(1-D)/fs)
.ends SC

```

The grounded switched capacitor of Figure 2.2b uses the following subckt:

```

* Switched capacitor with one grounded node
* -----
.subckt SCG 1p1 1p2 gnd
* Parameters:
* C=1p
* fs=1k
* D=0.5
.param Req={1/(fs*C)} Gmeq={1/Req}
R1 1p1 gnd {Req}
G1 gnd 1p1 1p2 gnd Laplace=Gmeq*exp(-s*D/fs)
R2 1p2 gnd {Req}
G2 gnd 1p2 1p1 gnd Laplace=Gmeq*exp(-s*(1-D)/fs)
.ends SCG

```

The OPAMPS need to be replaced by the switched OPAMP of Figure 2.2c which call the following subckt:

```

* Switched ideal OpAmp
* -----
.subckt SOPAMP in+p1 in-p1 outp1 in+p2 in-p2 outp2
* Parameters:
* Av=1E5
E1 outp1 0 in+p1 in-p1 {Av}
E2 outp2 0 in+p2 in-p2 {Av}
.ends SOPAMP

```

In many single-ended SC circuits the OPAMP has its positive terminal connected to ground. These OPAMPs need to be replaced by corresponding switched OPAMP of Figure 2.2d which uses the following subckt:

```

* Switched ideal OpAmp with grounded positive input
* -----
.subckt SOPAMPG in+ in-p1 outp1 in-p2 outp2
* Parameters:
* Av=1E5
E1 outp1 0 in+ in-p1 {Av}
E2 outp2 0 in+ in-p2 {Av}
.ends SOPAMPG

```

The use of this library will be illustrated by many examples presented below.

2.3 Approximation of time delay in ngspice

In the implementation of SC circuits with two non-overlapping phases for the simulation with LTSpice, we are using an ideal time delay $e^{-s\Delta T}$ where s is the Laplace variable, $\Delta T = D \cdot T$, with $T = 1/f_s$ the sampling period and D is the duty cycle (often equal to $D = 0.5$). This operator is available in LTSpice as `LAPLACE = exp(-s * D * T)` but unfortunately it is not available in ngspice. We can however use the XSpice `s_xfer` model which describes the transfer function given by a rational function in s with the order of the numerator m smaller than the order of the denominator n . There are various ways to approximate a constant delay with a rational function in s . The one that gives the best results is the Pade approximation [5]

$$e^{-s\Delta T} \cong \frac{\sum_{k=0}^m p_k \cdot (s \cdot \Delta T)^k}{\sum_{k=0}^n q_k \cdot (s \cdot \Delta T)^k} \quad (2.13)$$

The coefficients in the case $m = n$ are given by

$$q_k = \frac{(2n - k)!}{k! (n - k)!}, \quad (2.14)$$

$$p_k = (-1)^k \cdot q_k. \quad (2.15)$$

The corresponding transfer function of the ideal delay is

$$H(\omega) = e^{-j\omega \Delta T} \quad (2.16)$$

with a magnitude and phase given by

$$|H(\omega)| = 1, \quad (2.17)$$

$$\Phi(\omega) = \arg(H(\omega)) = -\omega \Delta T. \quad (2.18)$$

An ideal delay can be characterized by a constant phase delay defined as

$$\tau_\Phi(\omega) = -\frac{\Phi(\omega)}{\omega} = \Delta T \quad (2.19)$$

or group delay

$$\tau_{gd}(\omega) = -\frac{d\Phi(\omega)}{d\omega} = \Delta T \quad (2.20)$$

We can evaluate the coefficients for an order $n = 5$.

Table 2.1: Coefficients of $q[k]$ and $p[k]$ for $n = 5$.

n	p[k]	q[k]
0	30240	30240
1	-15120	15120
2	3360	3360
3	-420	420
4	30	30
5	-1	1

The approximations up to order 5 are simulated in LTSpice and compared to the ideal delay also simulated with LTSpice. The results are presented in Figure 2.3.

In the case of $D = 0.5$, the phase delay is equal to 0.5. We see that the approximations progressively extends the phase delay to higher frequency. Since we usually are only interested on frequencies up to the Nyquist frequency $f_2/2$, we observe that a 3rd-order approximation should already be fine.

We can simulate the delay block in ngspice using the `s_xfer` XSpice description. The simulation results are presented in Figure 2.4.

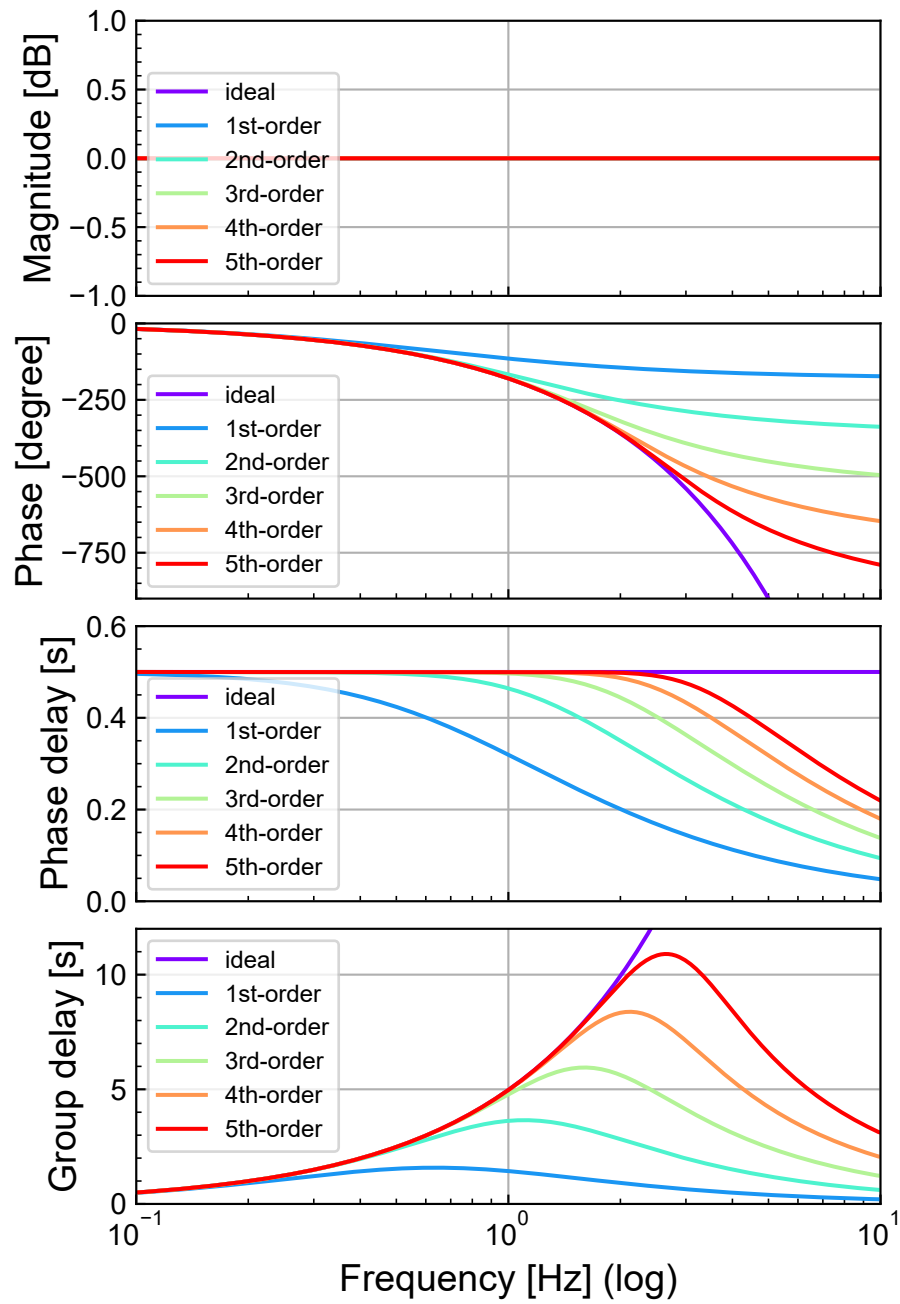


Figure 2.3: Comparison of the delay approximation to the ideal delay.

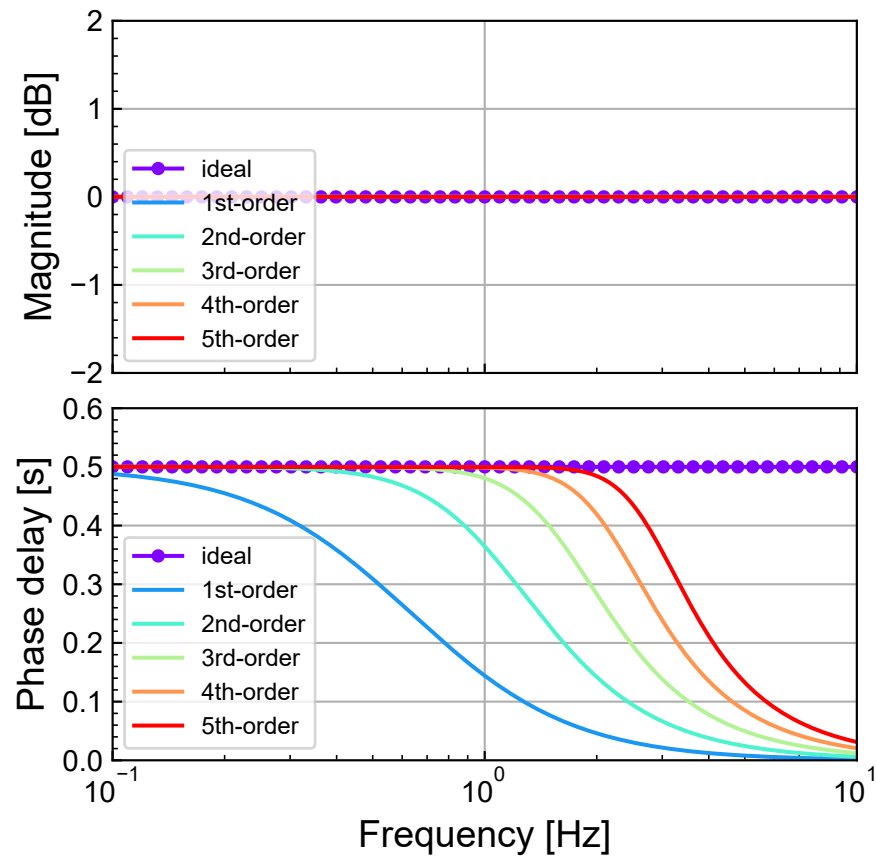


Figure 2.4: Delay approximation with ngspice.

3 Example 1: First-order passive low-pass filter

The simplest example is the implementation of a 1st-order passive RC low-pass filter as illustrated in the left schematic of Figure 3.1.

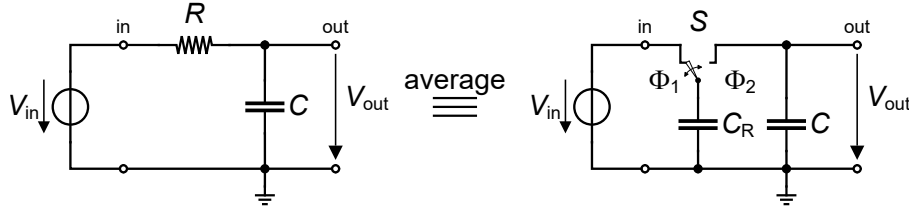


Figure 3.1: Equivalence between 1st-order passive RC and SC filter.

The transfer function of the continuous-time passive RC filter is given by

$$H_a(s) = \frac{1}{1 + s\tau} = \frac{1}{1 + s/\omega_c} \quad (3.1)$$

with $\tau = 1/\omega_c = RC$. The SC equivalent filter is shown on the right of Figure 3.1 where

$$C_R = \alpha \cdot C \quad (3.2)$$

with

$$\alpha = \frac{\omega_c}{f_s} = 2\pi \frac{f_c}{f_s}, \quad (3.3)$$

where f_s is the sampling frequency.

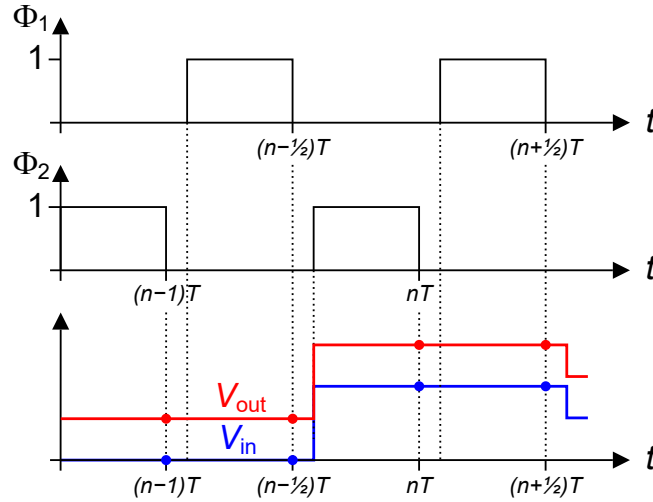


Figure 3.2: Phases and signals for the analysis of the passive SC filter.

Assuming that the output voltage during phase Φ_2 settles to its final value at the end of phase Φ_2 , we can write the charge conservation equation between the end of phase Φ_2 , i.e. time $t = nT$, and the end of phase Φ_1 , i.e. time $(n - 1/2)T$ as

$$(C + C_R) V_{out}(nT) = C_R V_{in}((n - 1/2)T) + C V_{out}((n - 1/2)T). \quad (3.4)$$

Assuming that the input and output voltages change only once per period as shown in Figure 3.2, we have

$$V_{in}((n - 1/2)T) = V_{in}((n - 1)T), \quad (3.5)$$

$$V_{out}((n - 1/2)T) = V_{out}((n - 1)T). \quad (3.6)$$

The above difference equation becomes

$$(C + C_R) V_{out}(nT) = C_R V_{in}((n - 1)T) + C V_{out}((n - 1)T), \quad (3.7)$$

Taking the z -transform leads to

$$(C + C_R) V_{out}(z) = z^{-1} [C_R V_{in}(z) + C V_{out}(z)] \quad (3.8)$$

which can be solved to derive the z -transfer function of the passive SC filter

$$H(z) = \frac{\alpha z^{-1}}{1 + \alpha - z^{-1}} = \frac{\alpha}{(1 + \alpha)z - 1} \quad (3.9)$$

with

$$\alpha = \frac{C_R}{C}. \quad (3.10)$$

As an example, we want to implement a 1st-order low-pass filter of Figure 3.1 with the parameters given in Table 3.1.

Table 3.1: Parameters for the 1st-order passive low-pass filter of Figure 3.1.

Specification	Symbol	Value	Unit
Cut-off frequency	f_c	1	kHz
Sampling frequency	f_s	100	kHz
Capacitance	C	1	pF
Capacitance ratio	$\alpha \triangleq \omega_c / f_s$	0.062832	-
Switched-capacitance	C_R	62.832	fF

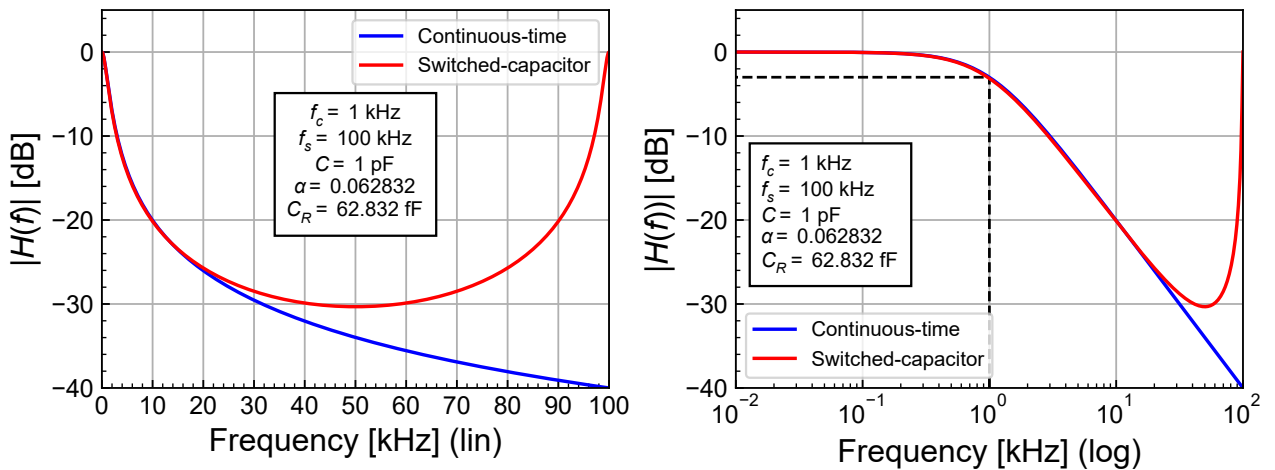


Figure 3.3: Transfer function magnitude of the 1st-order passive low-pass filter of Figure 3.1.

As expected, the magnitude of the transfer function shown in Figure 3.1 is periodic with a period $f_s = 100 \text{ kHz}$. From Figure 3.1, we see that the cut-off frequency of the SC filter is equal to that of the continuous-time (CT) filter. However, because of the sampled-data nature of the SC filter, the transfer function is periodic in f_s . The maximum attenuation is therefore only about 30 dB.

3.1 Simulations

3.1.1 LTSpice

For the LTSpice simulations we can use the schematic shown in Figure 3.4.

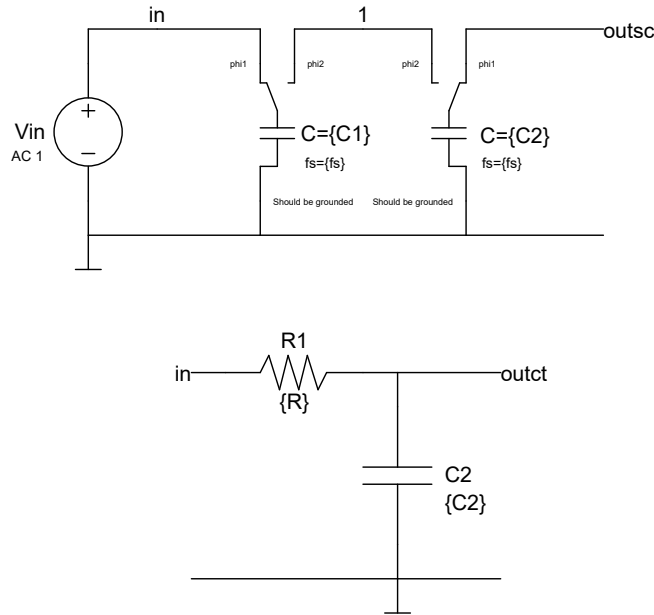


Figure 3.4: LTSpice schematic.

i Note

We may wonder why capacitor C_2 also needs to be modeled by a switched-capacitor in LTSpice despite the fact that it is not really switched. The reason is that we need to define two separate circuits, one that represents the circuit during phase Φ_1 and the other for phase Φ_2 . We cannot have a schematic node, for example node 1 in the above circuit, that is common to the circuit of phase Φ_1 and the circuit of phase Φ_2 . The two separate circuits are then coupled by the implementation of charge conservation between phase Φ_1 and Φ_2 .

We can now simulate the circuit in LTSpice with the same parameters as in Table 3.1.

With the linear x-axis in Figure 3.5, we can clearly see that the LTSpice AC simulation captures the sampled-data nature of the transfer function of the SC circuit which is now periodic with a period f_s . It then obviously deviates from the CT transfer function for frequencies above about $f_s/10$.

We can now simulate and plot the same circuit but with a log scale to check whether the cut-off frequency is correct.

The results shown in Figure 3.5 and Figure 3.6 show that the simulations perfectly match the theoretical results and that the cut-off frequency is correct and that the asymptotic slope of -20dB/dec above the cut-off frequency is correct as well, up to about $f_s/10$.

We now will now simulate the circuit of Figure 3.4 with the ngspice simulator.

3.1.2 ngspice

We first have a look at the simulations with a linear scale for the frequency axis.

From Figure 3.7, we see that the ngspice simulation perfectly matches the theoretical data.

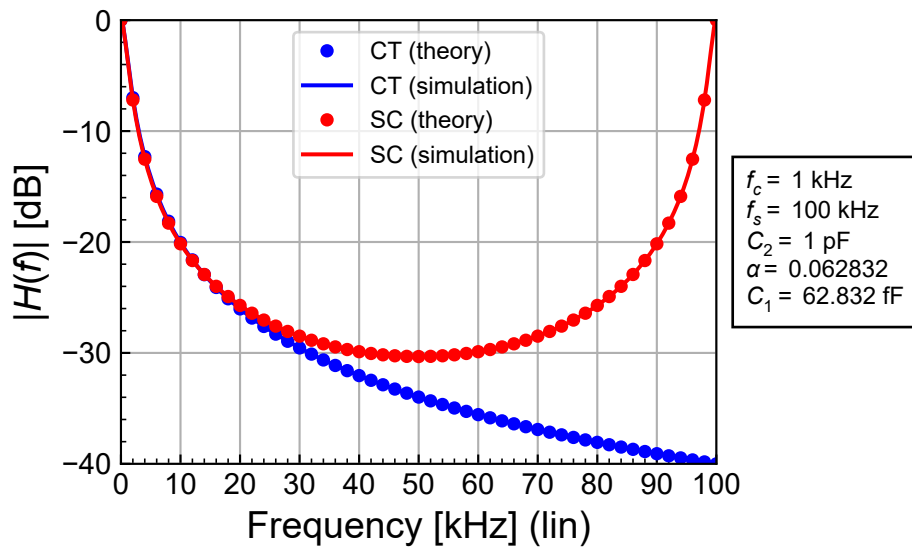


Figure 3.5: Transfer function magnitude of the simulated 1st-order passive low-pass filter of Figure 3.4 with linear x-axis.

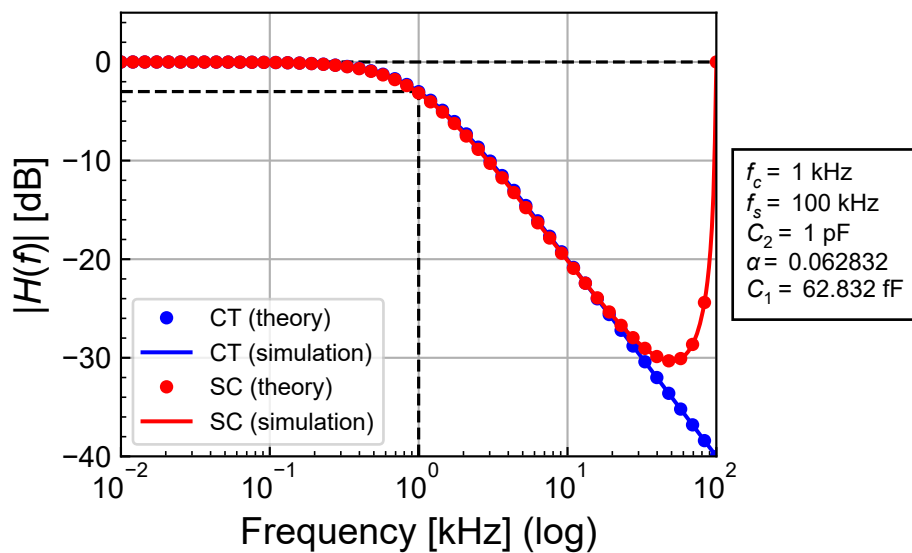


Figure 3.6: Transfer function magnitude of the simulated 1st-order low-pass filter of Figure 3.4 with log x-axis.

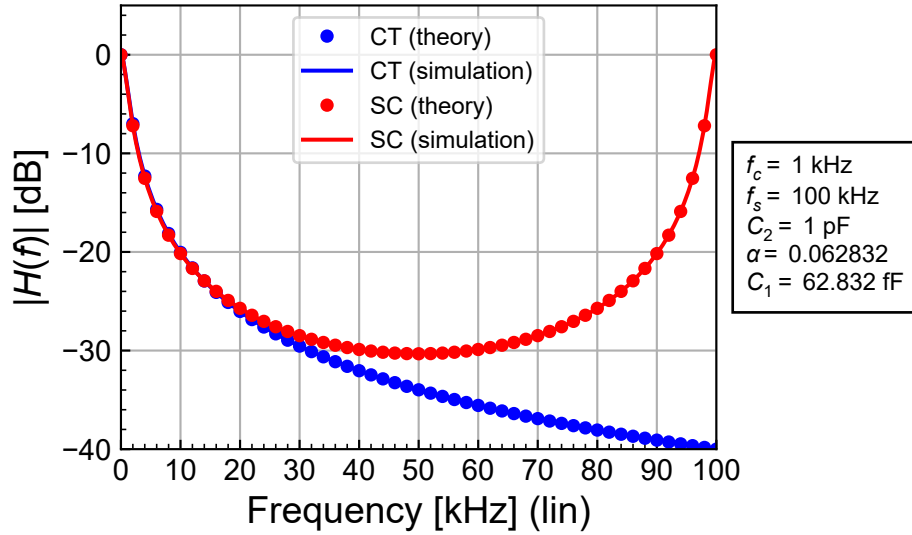


Figure 3.7: Transfer function magnitude of the simulated 1st-order low-pass filter compared to the passive RC circuit with linear x-axis.

We can check the effect of the various order for the delay model in ngspice.

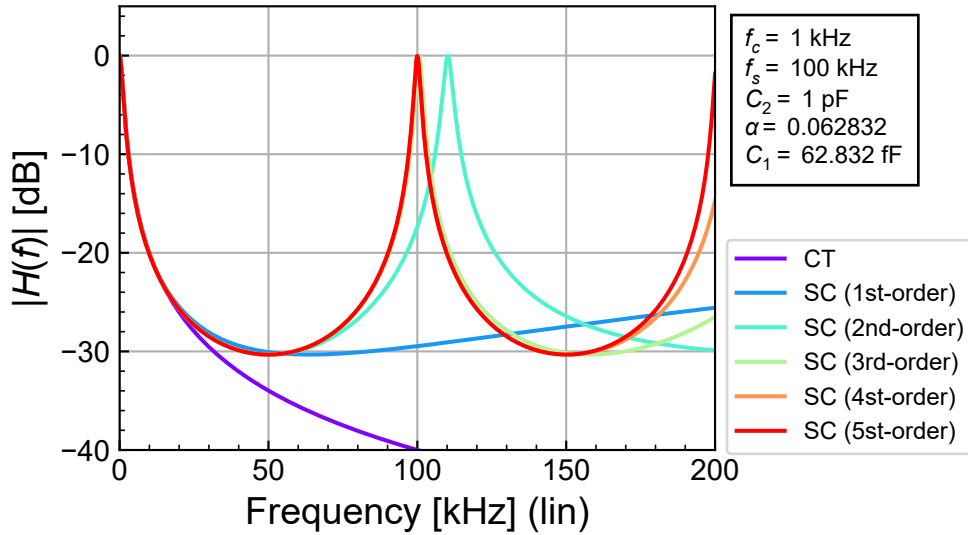


Figure 3.8: ngspice transfer function magnitude simulation of the 1st-order passive low-pass filter with different delay approximation orders.

We can observe in Figure 3.8 that the 1st-order delay model shows a large discrepancy and is therefore not sufficient. The 2nd-order delay model already does a good job up to the Nyquist frequency which is what we need. The 3rd-order and 4th-order delay models show discrepancy above $3f_s/2$. We will keep the 5th-order delay model since it does not penalize the simulation time.

The plot of Figure 3.9 shows that the ngspice simulation perfectly matches the theoretical result and that the cut-off frequency is correct and that the asymptotic slope of -20dB/dec above the cut-off frequency is correct as well, up to about $f_s/10$.

We can now proceed with the simplest active SC filter, namely a 1st-order LP filter.

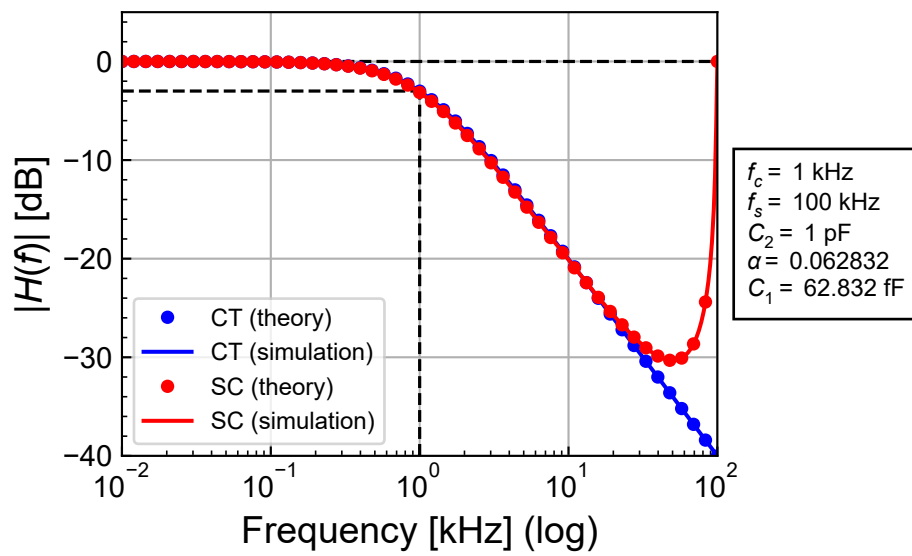


Figure 3.9: Transfer function magnitude of the simulated 1st-order low-pass filter compared to the passive RC circuit with log x-axis.

4 Example 2: First-order active low-pass filter

The schematic of the general 1st-order SC section is shown in Figure 4.1.

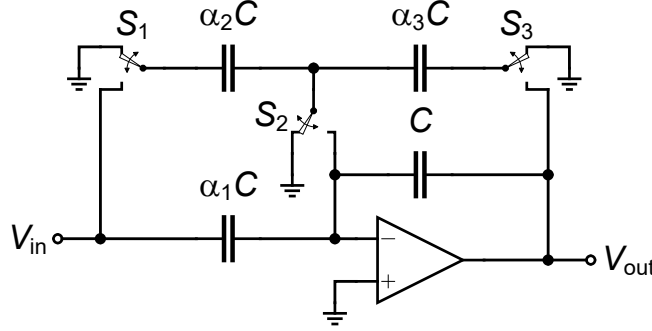


Figure 4.1: 1st-order LP filter with the zero inside the unit circle.

The z -transfer function is given by

$$H(z) = -\frac{(\alpha_1 + \alpha_2)z - \alpha_1}{(1 + \alpha_3)z - 1} \quad (4.1)$$

From the above z -transfer function, we observe that the zero $z_z = \alpha_1/(\alpha_1 + \alpha_2) < 1$ is always inside the unit circle. The corresponding approximate s -domain transfer assuming $z \cong 1 + sT$ is given by

$$H_a(s) \cong -K \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p} \quad (4.2)$$

The approximate design equations for $\omega_z T \ll 1$ and $\omega_p T \ll 1$ are given by

$$\alpha_1 \cong K, \quad (4.3)$$

$$\alpha_2 \cong K \omega_z T, \quad (4.4)$$

$$\alpha_3 \cong \omega_p T. \quad (4.5)$$

With the circuit of Figure 4.1, we cannot disable the zero to implement a simple LP transfer function. Another 1st-order section having the zero outside the unit circle is shown in Figure 4.2.

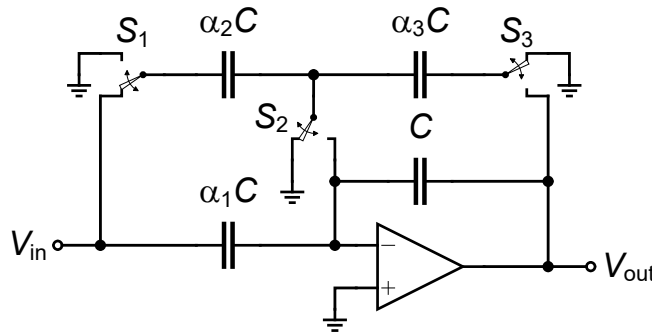


Figure 4.2: 1st-order LP filter with the zero outside the unit circle.

The z -transfer function is given by

$$H(z) = -\frac{\alpha_1 z - (\alpha_1 + \alpha_2)}{(1 + \alpha_3)z - 1} \quad (4.6)$$

From the above z -transfer function, we observe that the zero $z_z = 1 + \alpha_2/\alpha_1 > 1$ is now outside the unit circle. The corresponding approximate s -domain transfer assuming $z \cong 1 + sT$ is given by

$$H_a(s) \cong K \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p} \quad (4.7)$$

The approximate design equations for $\omega_z T \ll 1$ and $\omega_p T \ll 1$ are given by

$$\alpha_1 \cong K \frac{\omega_p T}{\omega_z T}, \quad (4.8)$$

$$\alpha_2 \cong K \omega_p T, \quad (4.9)$$

$$\alpha_3 \cong \omega_p T. \quad (4.10)$$

A LP transfer function without zero can now be implemented setting $\omega_z T \rightarrow \infty$ by choosing $\alpha_1 = 0$. If additionally the gain in the passband is unity $K = 1$, then $\alpha_2 = \alpha_3 = \alpha$ resulting in the schematic shown in Figure 4.3.

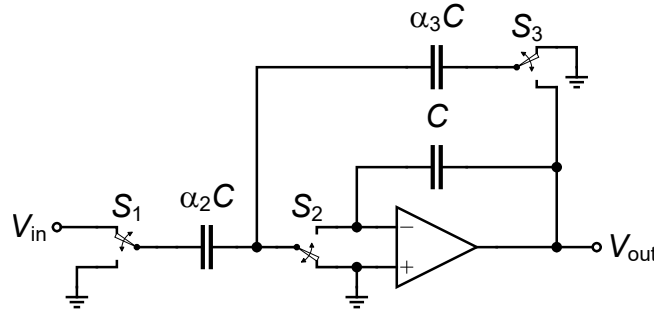


Figure 4.3: 1st-order LP filter.

As an example, we want to implement a 1st-order LP filter with the parameters given in Table 4.1.

Table 4.1: Parameters for the 1st-order low-pass filter of Figure 4.3.

Specification	Symbol	Value	Unit
Scaling factor	K	1	-
Cut-off frequency	f_c	1	kHz
Clock frequency	f_{ck}	200	kHz
Integrating capacitance	C	3.3	pF
Capacitance ratio	$\alpha_2 = \alpha_3 = \alpha = \omega_c T$	0.031416	-
Switched-capacitance	$C_2 = \alpha \cdot C$	103.673	fF
Switched-capacitance	$C_3 = \alpha \cdot C$	103.673	fF

4.1 Simulations

For the Spice simulation we will assume that the OPAMP have a DC gain $A = 100$ and infinite bandwidth.

4.1.1 LTSpice

The 1st-order LP SC filter of Figure 4.3 can be simulated in LTSpice using the dedicated library. The corresponding schematic is shown below.

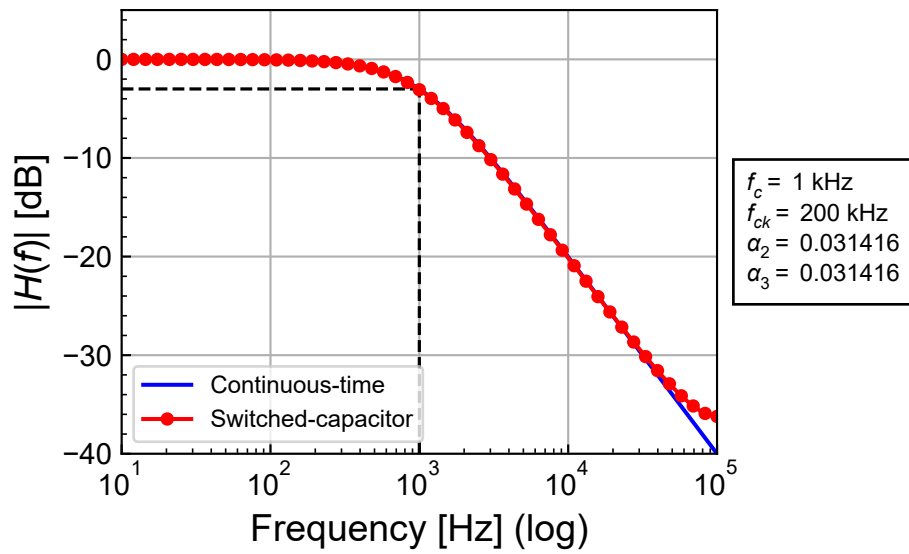


Figure 4.4: Theoretical transfer function of the 1st-order active low-pass filter of Figure 4.3.

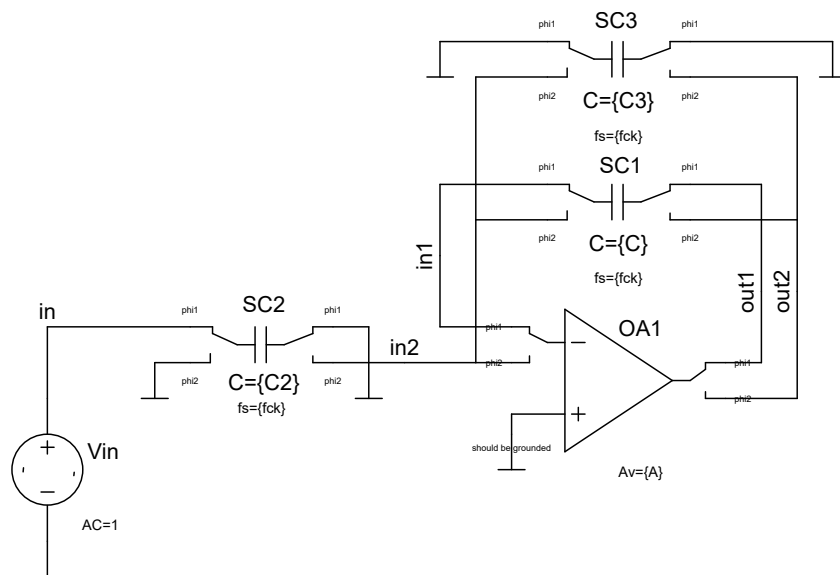


Figure 4.5: Schematic of the 1st-order LP SC filter for LTSpice simulation.

Notice that the integrating capacitor C , which is actually not switched, is also modelled by a switched-capacitor (SC1 in the above schematic). As explained above, this is because the circuits during phase Φ_1 and Φ_2 need to be completely separated without any common nodes except the ground. We also need a special amplifier that has two different negative inputs and two different outputs, one for phase Φ_1 and the other for phase Φ_2 .

The simulation result is presented in Figure 4.6 and compared to the theoretical transfer and the continuous-time (CT) equivalent. We see that the simulated transfer function perfectly matches the theoretical transfer function.

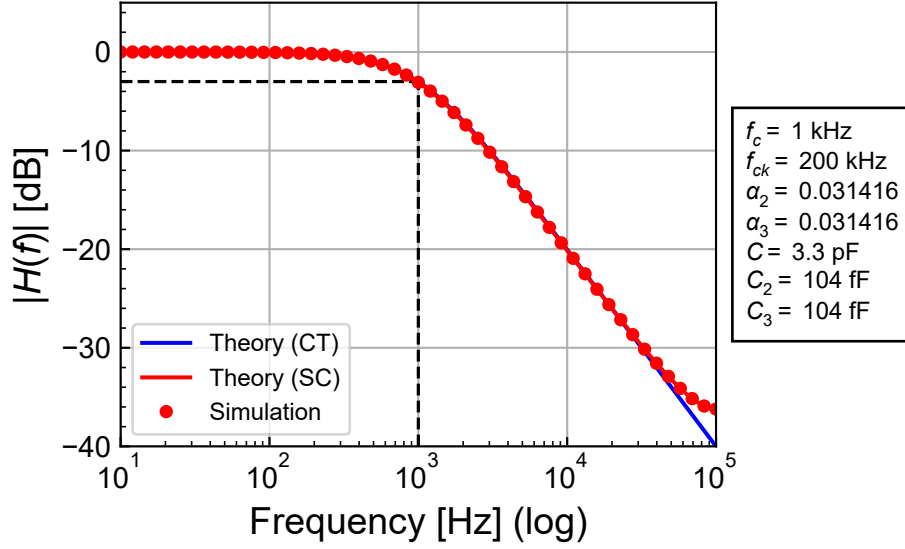


Figure 4.6: Simulated transfer function of the active 1st-order low-pass SC filter of Figure 4.5.

We now will simulate the same circuit with ngspice.

4.1.2 ngspice

We simulate the same circuit of Figure 4.5 with ngspice. The simulation result is presented in Figure 4.7 and compared to the theoretical and CT equivalent transfer functions. We can observe that the simulated transfer function perfectly matches the theoretical transfer function.

As shown in Figure 4.8, the ngspice simulation results perfectly match the LTSpice results.

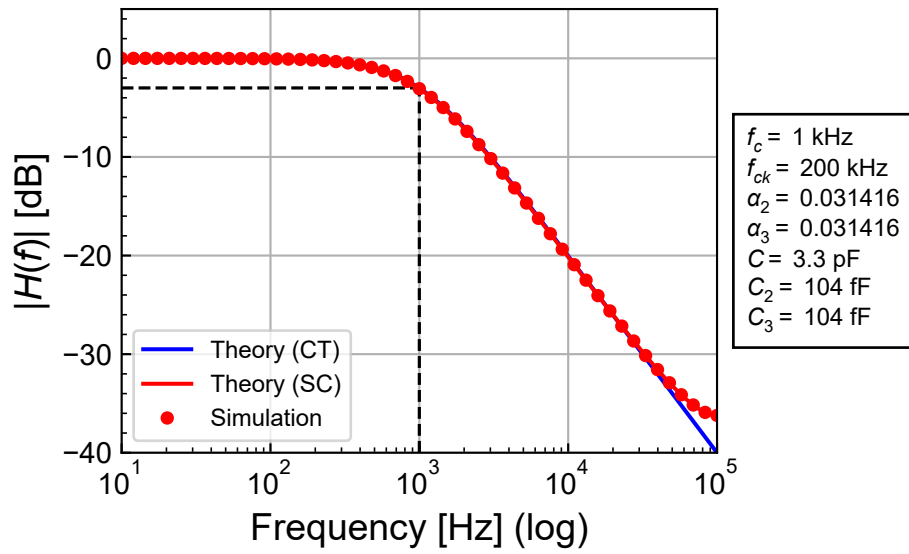


Figure 4.7: Simulated transfer function of the active 1st-order low-pass SC filter of Figure 4.5.

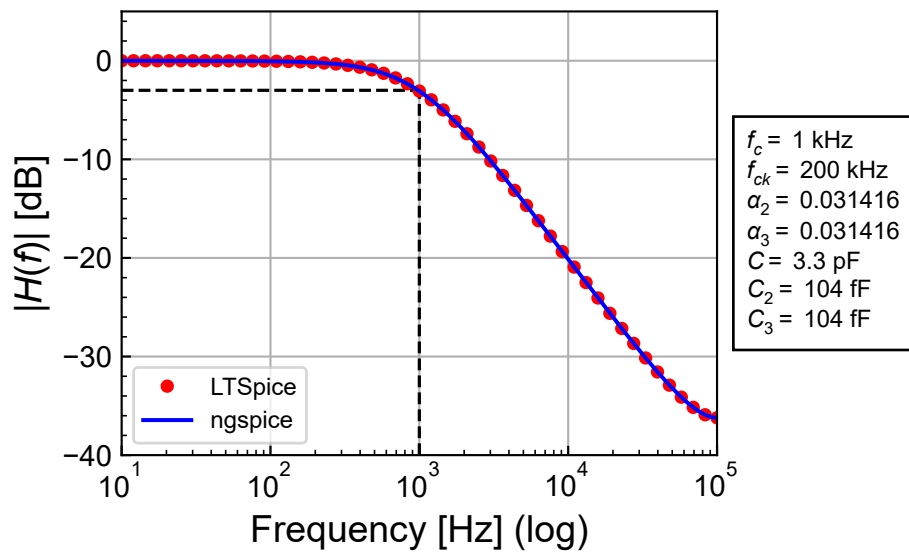
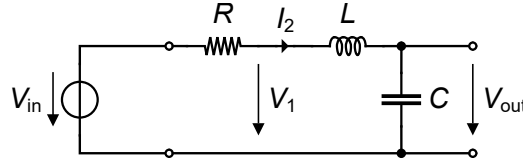


Figure 4.8: Simulated transfer function of the active 1st-order low-pass SC filter of Figure 4.5.

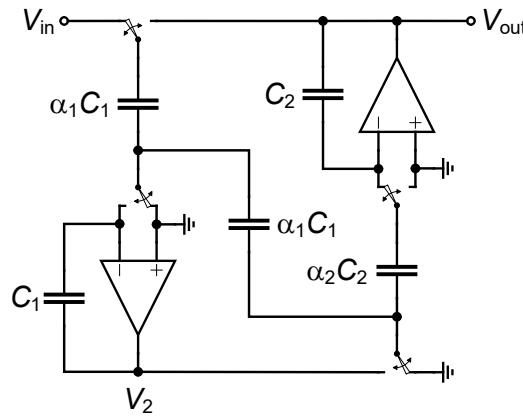
5 Example 3: Second-order active low-pass filter

Figure 5.1: 2nd-order LC ladder.

The next example is the simplest LC ladder filter shown in Figure 5.1 which includes only one inductor and one capacitor. In this case the load termination is infinite and therefore there is no 6 dB loss to correct for. The LC ladder component values for implementing a Butterworth approximation with a -3 dB cut-off frequency at $f_c = 20\text{ kHz}$ are given in Table 5.1.

Table 5.1: Component values of the 3rd-order LC filter for implementing a Butterworth approximation.

Symbol	Value	Unit
R	1	Ω
L	5.627	μH
C	11.25	μF

Figure 5.2: 2nd-order SC LP filter.

It can be shown that the transfer function can be implemented by the SC filter shown in Figure 5.2. From charge conservation analysis, it can be shown that the theoretical transfer function is given by

$$H_{SC}(z) = \frac{a_1 z}{b_2 z^2 + b_1 z + b_0} \quad (5.1)$$

with

$$a_1 = \alpha_1 \alpha_2, \quad (5.2)$$

$$b_0 = 1, \quad (5.3)$$

$$b_1 = \alpha_1 \alpha_2 - \alpha_1 - 2, \quad (5.4)$$

$$b_2 = \alpha_1 + 1. \quad (5.5)$$

where

$$\alpha_1 = \frac{1}{f_s \tau_1}, \quad (5.6)$$

$$\alpha_2 = \frac{1}{f_s \tau_2}, \quad (5.7)$$

with

$$\tau_1 = \frac{L}{R}, \quad (5.8)$$

$$\tau_2 = R \cdot C. \quad (5.9)$$

The integrators time constants and capacitance ratios for a clock frequency $f_{ck} = 2 \text{ MHz}$ are given in Table 5.2.

Table 5.2: Capacitance ratios of the 2nd-order Butterworth LP filter of Figure 5.2.

Symbol	Value	Unit
τ_1	5.627	μs
τ_2	11.25	μs
α_1	0.088857	-
α_2	0.044444	-

The theoretical transfer function (7.1) is compared to that of the LC passive filter in Figure 5.3. We see a perfect agreement except at high frequency where we observe the deviation due to the sampled-data nature of the SC filter.

We can now check the design by LTspice and ngspice simulations.

5.1 Simulations

5.1.1 LTSpice

The 2nd-order SC Butterworth LP filter can be simulated in LTSpice using the schematic shown in Figure 5.4. The simulation result are compared to the theoretical transfer function in Figure 5.5. We see a perfect match even at high frequency.

Table 5.3: Component values of the 2nd-order active low-pass SC filter of Figure 5.4.

Symbol	Value	Unit
A	100	dB
f_{ck}	2	MHz
C_1	3.3	pF
C_2	3.3	pF
α_1	0.088857	-
α_2	0.044444	-
$C_{11} = \alpha_1 C_1$	293	fF
$C_{12} = \alpha_1 C_1$	293	fF
$C_2 = \alpha_2 C_2$	147	fF
$C_{21} = \alpha_2 C_2$	147	fF

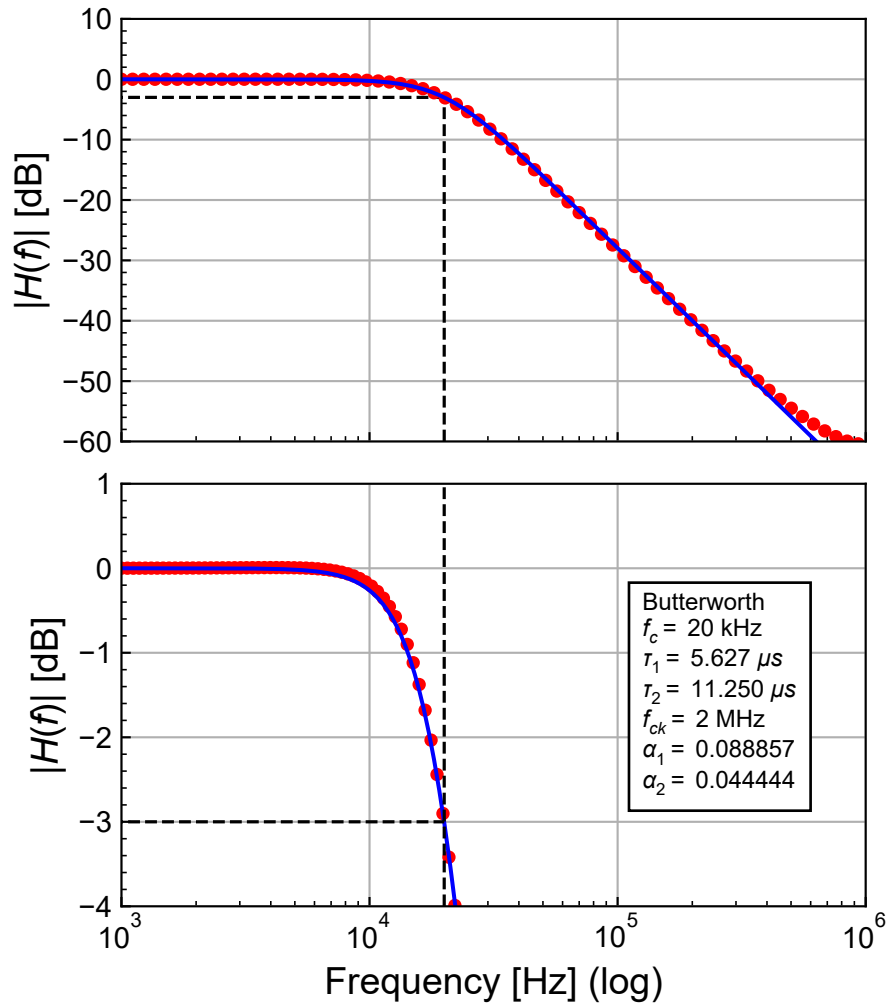


Figure 5.3: Theoretical transfer function magnitude of the 2nd-order active low-pass SC filter of Figure 5.2.

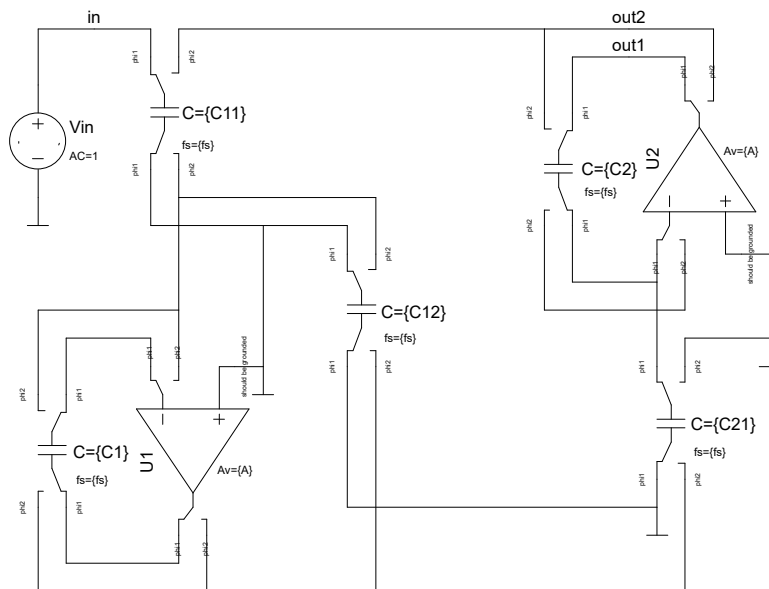


Figure 5.4: Schematic of the 2nd-order LP SC filter used for LTSpice simulations

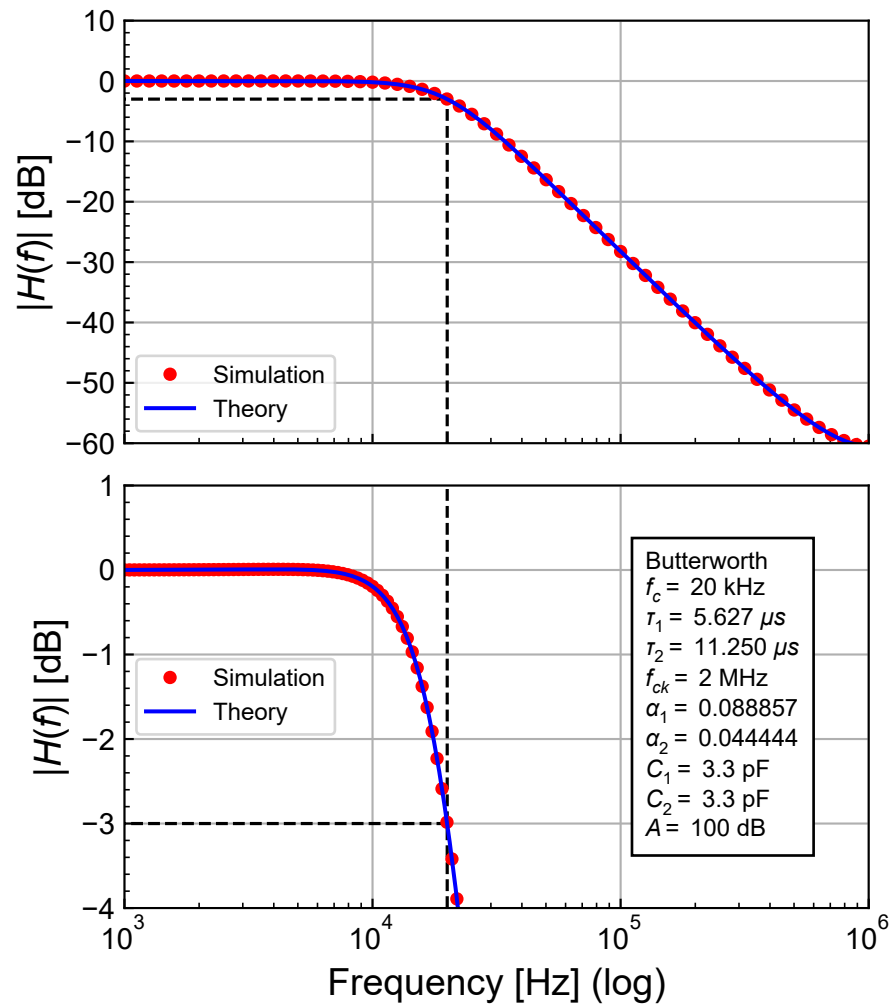


Figure 5.5: Simulated transfer function of the active 3rd-order low-pass SC filter of .

5.1.2 ngspice

The ngspice simulation is performed with the same circuit as the LTSpice circuit of Figure 5.4 with the same component values as in Table 6.3. The ngspice simulation result is presented in Figure 5.6. Similarly to the LTSpice, we see a perfect match between the simulated and the theoretical transfer functions.

Table 5.4: Component values of the 2nd-order active low-pass SC filter of Figure 5.4.

Symbol	Value	Unit
A	20	dB
f_{ck}	2	MHz
C_1	3.3	pF
C_2	3.3	pF
α_1	0.088857	-
α_2	0.044444	-
$C_{11} = \alpha_1 C_1$	293	fF
$C_{12} = \alpha_1 C_1$	293	fF
$C_2 = \alpha_2 C_2$	147	fF
$C_{21} = \alpha_2 C_2$	147	fF

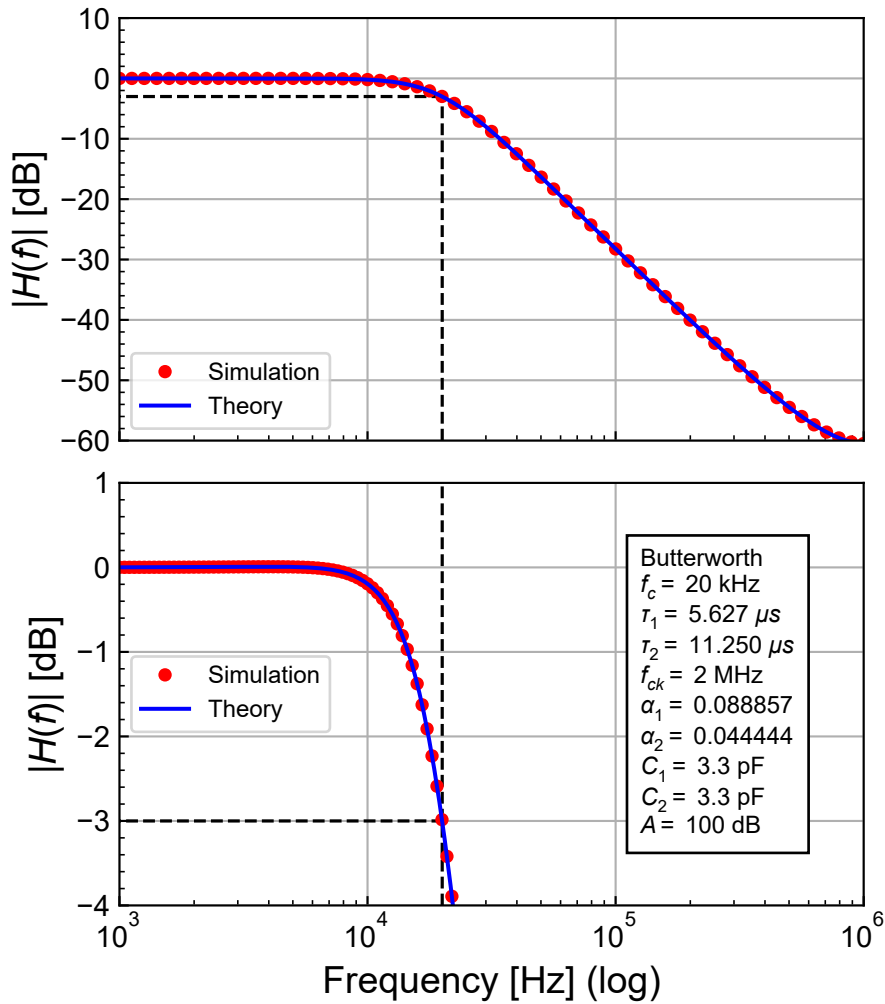


Figure 5.6: Simulated transfer function of the active 2nd-order low-pass SC filter of Figure 5.4.

6 Example 4: Third-order active low-pass filter

The third example is the 3rd-order low-pass filter shown in Figure 6.1.

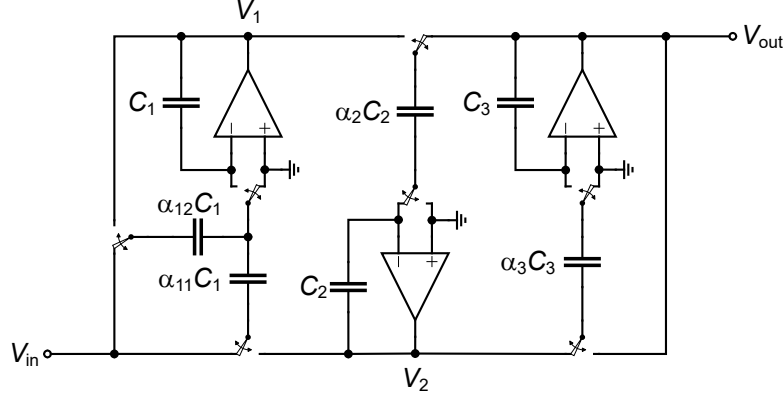


Figure 6.1: Complete 3rd-order SC LP filter including the -6 dB DC gain correction.

From charge conservation analysis, it can be shown that the theoretical transfer function is given by

$$H(z) = \frac{a_2 z^2}{b_3 z^3 + b_2 z^2 + b_1 z + b_0} \quad (6.1)$$

with

$$a_2 = (\alpha_{11} + \alpha_{12}) \alpha_2 \alpha_3, \quad (6.2)$$

$$b_0 = -1, \quad (6.3)$$

$$b_1 = 3 + \alpha_{12} - \alpha_{11} \alpha_2 + \alpha_3 - \alpha_2 \alpha_3, \quad (6.4)$$

$$b_2 = -3 - 2 \alpha_{12} + \alpha_{11} \alpha_2 - 2 \alpha_3 - \alpha_{12} \alpha_3 + \alpha_2 \alpha_3 + \alpha_{11} \alpha_2 \alpha_3 + \alpha_{12} \alpha_2 \alpha_3, \quad (6.5)$$

$$b_3 = (1 + \alpha_{12})(1 + \alpha_3). \quad (6.6)$$

The specifications of the filter are given in Table 6.1 .

Table 6.1: Specifications of the 3rd-order active low-pass filter.

Specification	Symbol	Value	Unit
Cut-off frequency	f_p	20	kHz
Stop-band frequency	f_s	120	kHz
Clock frequency	f_{ck}	2	MHz
Pass-band gain	G_p	-1	dB
Stop-band gain	G_s	-40	dB

The capacitance ratios for a Chebyshev approximation and a clock frequency $f_s = 2 \text{ MHz}$ are given in Table 6.2.

Table 6.2: Capacitance ratios of the 3rd-order active low-pass SC filter of Figure 6.1.

Symbol	Value	Unit
τ_1	16.1032	μs
τ_2	7.91082	μs
τ_3	16.1032	μs
f_s	2	MHz
α_{11}	0.03105	-
α_{12}	0.03105	-
α_2	0.063205	-
α_3	0.03105	-

The transfer function magnitude corresponding to the parameters given in Table 6.2 is shown in Figure 6.2.

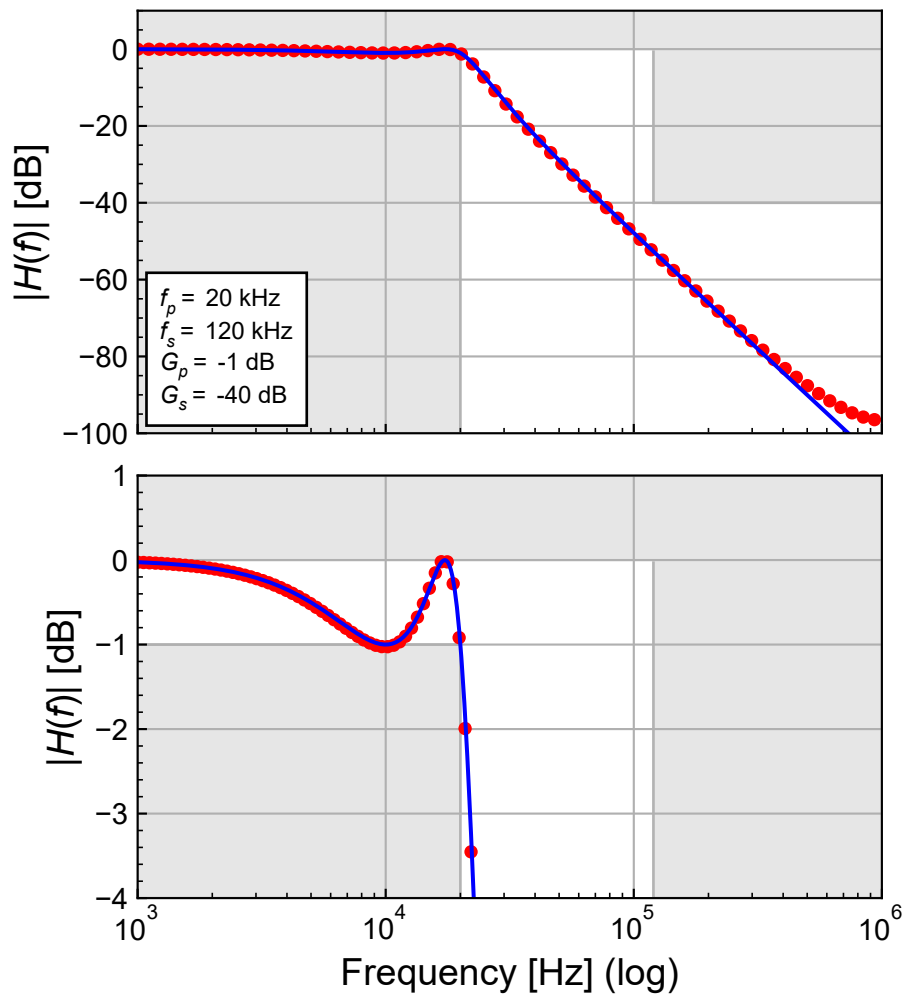


Figure 6.2: Theoretical transfer function magnitude of the 3rd-order active low-pass SC filter of Figure 6.1.

6.1 Simulations

6.1.1 LTSpice

The LTSpice simulations are done with the schematic shown in Figure 6.3 with the capacitance values and capacitance ratios given in Table 6.3.

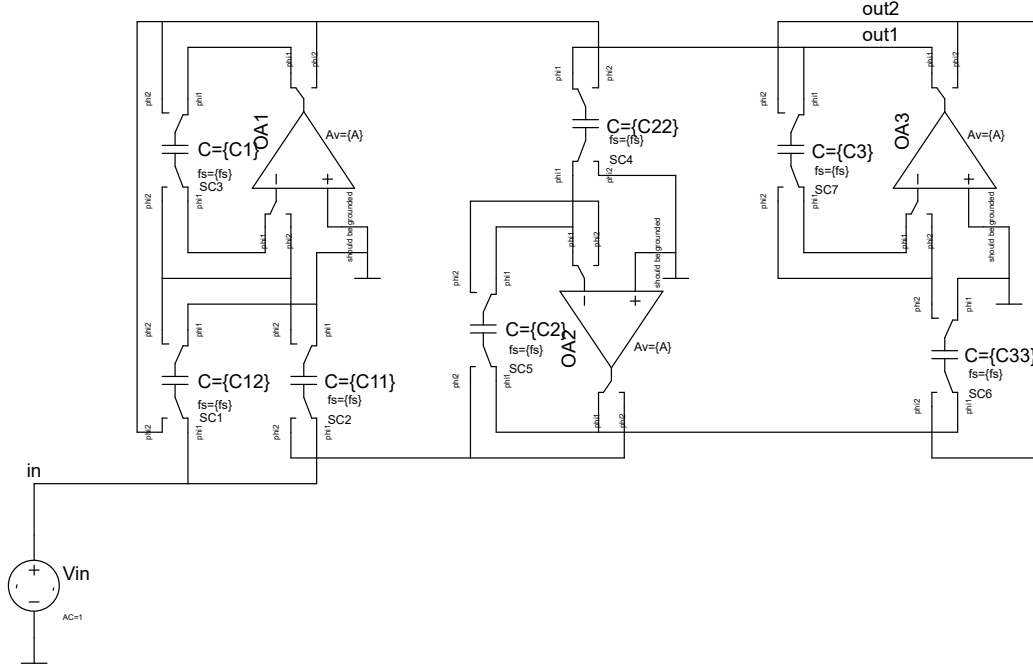


Figure 6.3: Schematic used for the LTSpice simulation.

The simulated magnitude of the transfer function is compared to the theoretical one in Figure 6.4.

Table 6.3: Component values of the 3rd-order active low-pass SC filter of Figure 6.3.

Symbol	Value	Unit
A	100	dB
f_{ck}	2	MHz
α_{11}	0.03105	-
α_{12}	0.03105	-
α_2	0.063205	-
α_3	0.03105	-
C_1	3.3	pF
C_2	3.3	pF
C_3	3.3	pF
$C_{11} = \alpha_{11} C_1$	102	fF
$C_{12} = \alpha_{12} C_1$	102	fF
$C_{22} = \alpha_2 C_2$	209	fF
$C_{33} = \alpha_3 C_3$	102	fF

From Figure 6.4, we see that the LTSpice simulation perfectly matches the theoretical transfer function.

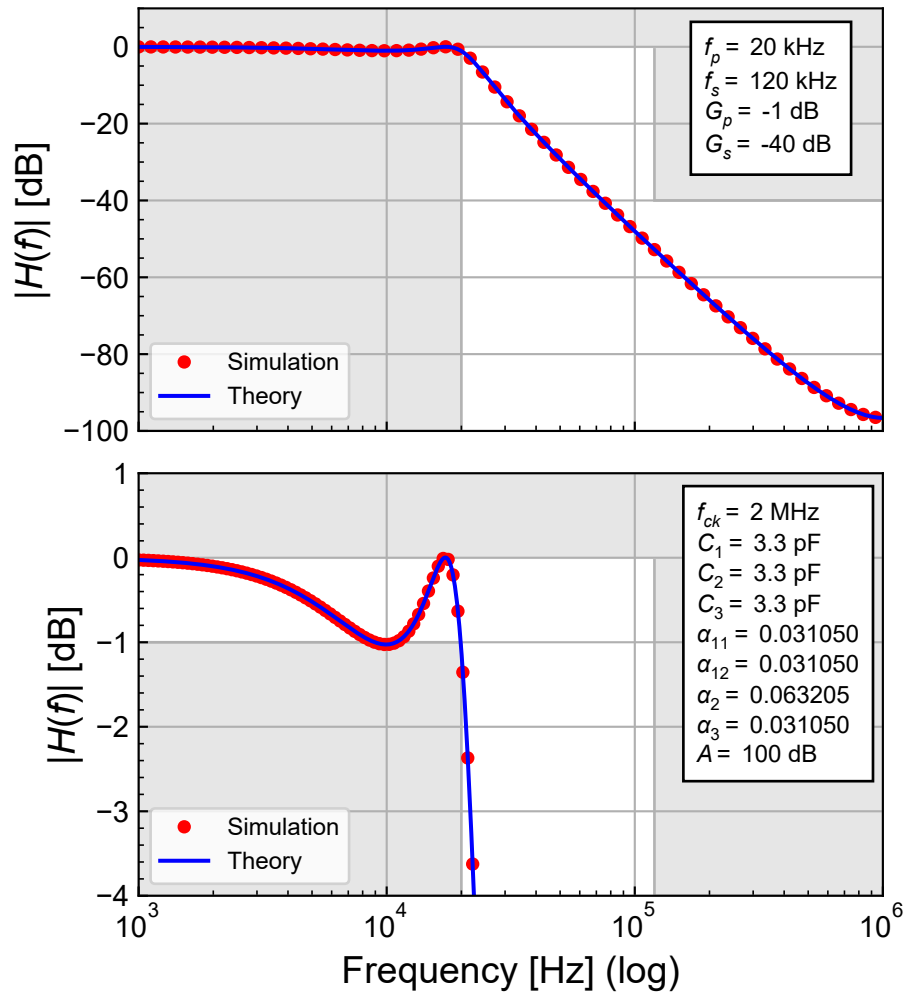


Figure 6.4: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

6.1.2 ngspice

The ngspice simulation is performed with the same circuit as the LTSpice circuit of Figure 6.3 with the same component values of Table 6.3. The ngspice simulation result is presented in Figure 6.5. Similarly to the LTSpice, we see a perfect match between the simulated and the theoretical transfer functions.

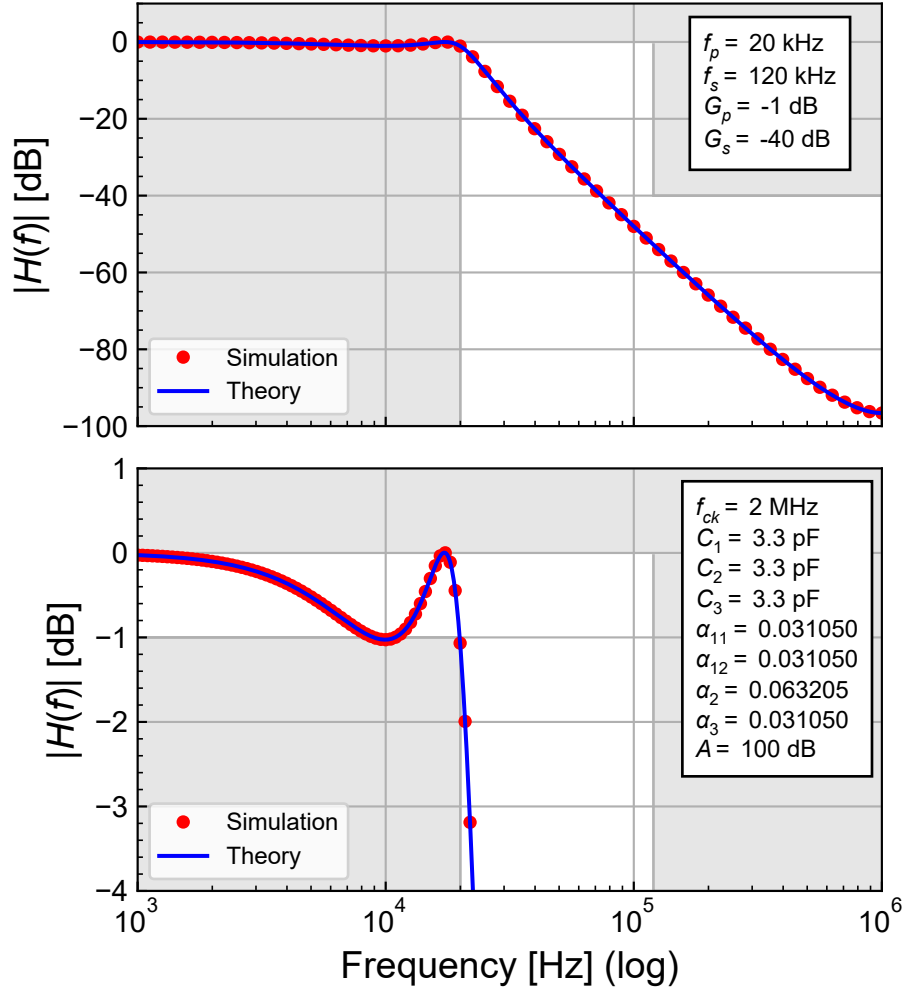


Figure 6.5: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

7 Example 5: Third-order elliptic low-pass filter

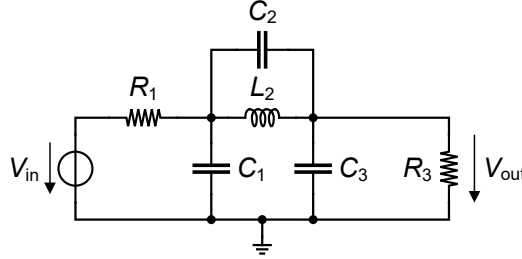


Figure 7.1: LC 3rd-order elliptic LP filter.

The last example is a 3rd-order elliptic low-pass filter including transmission zeroes. It is based on the passive LC filter shown in Figure 7.1. The component values to satisfy the specifications given in Table 7.1 are given in Table 7.2.

Table 7.1: Specifications of the 3rd-order active low-pass elliptic filter.

Specification	Symbol	Value	Unit
Cut-off frequency	f_p	20	kHz
Stop-band frequency	f_s	120	kHz
Clock frequency	f_{ck}	2	MHz
Pass-band gain	G_p	-1	dB
Stop-band gain	G_s	-40	dB


Table 7.2: Component values of the 3rd-order LC filter of Figure 7.1.

Symbol	Value	Unit
C_1	15.19	μF
C_2	1.157	μF
C_3	15.19	μF
L_2	7.196	μH
R_1	1	Ω
R_3	1	Ω

It can be shown that the corresponding SC filter achieving the desired elliptic transfer function is obtained as shown in Figure 7.2. It is basically identical to the SC low-pass filter of Figure 6.1 to which the two additional non-switched capacitors $\beta_1 C_1$ and $\beta_3 C_3$ have been added to realize the transmission zero.

From charge conservation analysis, it can be shown that the theoretical z -transfer function is given by

$$H(z) = \frac{a_3 z^3 + a_2 z^2 + a_1 z + a_0}{b_3 z^3 + b_2 z^2 + b_1 z + b_0} \quad (7.1)$$

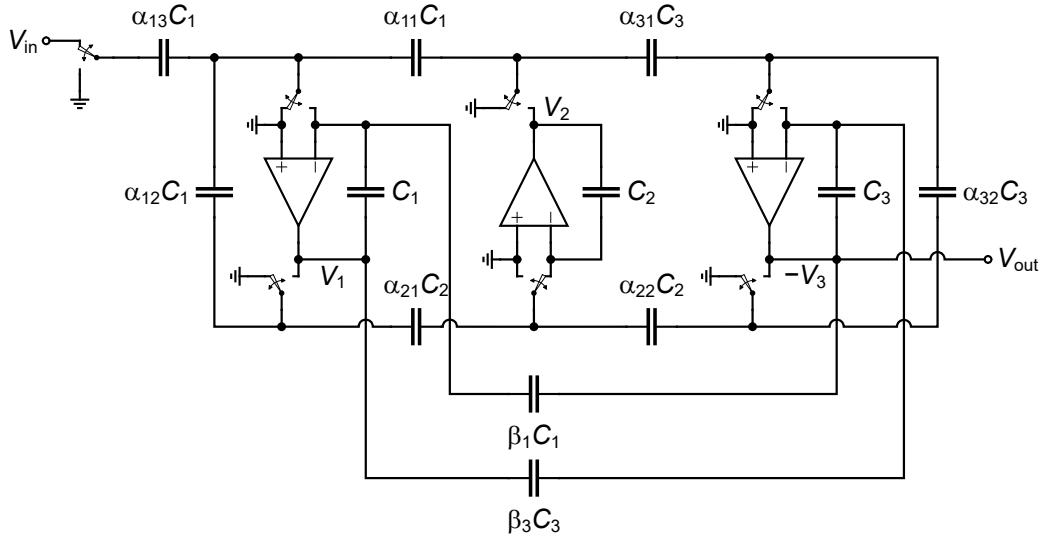Figure 7.2: 3rd-order SC elliptic LP filter.

with

$$a_0 = 0, \quad (7.2)$$

$$a_1 = \alpha_{13} \beta_3, \quad (7.3)$$

$$a_2 = \alpha_{13} (\alpha_{21} \alpha_{31} - 2 \beta_3), \quad (7.4)$$

$$a_3 = \alpha_{13} \beta_3, \quad (7.5)$$

$$b_0 = 1 - \beta_1 \beta_3, \quad (7.6)$$

$$b_1 = -3 - \alpha_{12} + \alpha_{11} \alpha_{21} + \alpha_{22} \alpha_{31} - \alpha_{32} - \alpha_{21} \alpha_{31} \beta_1 - \alpha_{11} \alpha_{22} \beta_3 + 3 \beta_1 \beta_3, \quad (7.7)$$

$$b_2 = 3 + 2 \alpha_{12} - \alpha_{11} \alpha_{21} - \alpha_{22} \alpha_{31} - \alpha_{12} \alpha_{22} \alpha_{31} \quad (7.8)$$

$$+ 2 \alpha_{32} + \alpha_{12} \alpha_{32} - \alpha_{11} \alpha_{21} \alpha_{32} + \alpha_{21} \alpha_{31} \beta_1 + \alpha_{11} \alpha_{22} \beta_3 - 3 \beta_1 \beta_3, \quad (7.9)$$

$$b_3 = -1 - \alpha_{12} - \alpha_{32} - \alpha_{12} \alpha_{32} + \beta_1 \beta_3. \quad (7.10)$$

where

$$\alpha_{11} = \frac{1}{f_s \tau_1}, \quad (7.11)$$

$$\alpha_{12} = \alpha_{11}, \quad (7.12)$$

$$\alpha_{13} = 2 \alpha_{11}, \quad (7.13)$$

$$\alpha_{21} = \frac{1}{f_s \tau_2}, \quad (7.14)$$

$$\alpha_{22} = \alpha_{21}, \quad (7.15)$$

$$\alpha_{31} = \frac{1}{f_s \tau_3}, \quad (7.16)$$

$$\alpha_{32} = \alpha_{31}, \quad (7.17)$$

$$\beta_1 = \frac{C_2}{C_2'}, \quad (7.18)$$

$$\beta_3 = \frac{C_2}{C_3'}, \quad (7.19)$$

with

$$\tau_1 = R_1 \cdot C_1', \quad (7.20)$$

$$\tau_2 = \frac{L_2}{R_1}, \quad (7.21)$$

$$\tau_3 = R_1 \cdot C_3', \quad (7.22)$$

and

$$C'_2 = C_1 + C_2, \quad (7.23)$$

$$C'_3 = C_3 + C_2. \quad (7.24)$$

The SC filter capacitance ratios for achieving the specification of Table 7.1 with a clock frequency $f_s = 2 \text{ MHz}$ are given in Table 7.3. We can observe that the capacitance ratios are close but not equal to those of the 3rd-order SC low-pass filter without transmission zeroes given in Table 6.2.

Table 7.3: Capacitance ratios of the 3rd-order SC elliptic filter of Figure 7.2.

Symbol	Value	Unit
τ_1	16.347	μs
τ_2	7.196	μs
τ_3	16.347	μs
f_{ck}	2	MHz
α_{11}	0.030587	-
α_{12}	0.030587	-
α_{13}	0.061173	-
α_{21}	0.069483	-
α_{22}	0.069483	-
α_{31}	0.030587	-
α_{32}	0.030587	-
β_1	0.070778	-
β_3	0.070778	-

The theoretical transfer function (7.1) is compared to that of the LC passive filter corrected for the -6 dB loss in Figure 7.3. We see a perfect agreement except at high frequency where we observe the deviation due to the sampled-data nature of the SC filter.

We can now check the design by LTspice and ngspice simulations.

7.1 Simulations

7.1.1 LTSpice

The 3rd-order SC elliptic LP filter can be simulated in LTSpice using the schematic shown in Figure 7.4 with the component values given in Table 7.4.

Table 7.4: Component values of the 3rd-order active low-pass SC filter of Figure 6.3.

Symbol	Value	Unit
A	100	dB
f_{ck}	2	MHz
α_{11}	0.030587	-
α_{12}	0.030587	-
α_{13}	0.061173	-
α_{21}	0.069483	-
α_{22}	0.069483	-
α_{31}	0.030587	-
α_{32}	0.030587	-

Table 7.4: Component values of the 3rd-order active low-pass SC filter of Figure 6.3.

Symbol	Value	Unit
β_1	0.070778	-
β_3	0.070778	-
C_1	3.3	pF
C_2	3.3	pF
C_3	3.3	pF
$C_{11} = \alpha_{11} C_1$	101	fF
$C_{12} = \alpha_{12} C_1$	101	fF
$C_{13} = \alpha_{13} C_1$	202	fF
$C_{14} = \beta_1 C_1$	234	fF
$C_{21} = \alpha_{21} C_2$	229	fF
$C_{22} = \alpha_{22} C_2$	229	fF
$C_{31} = \alpha_{31} C_3$	101	fF
$C_{32} = \alpha_{32} C_3$	101	fF
$C_{33} = \beta_3 C_3$	234	fF

The simulated transfer function is compared to the theoretical one in Figure 7.5. Again we see a perfect match.

Figure 7.6 shows the transfer functions between the input and the output of the various OPAMPs corresponding to voltages V_1 , V_2 and V_3 in Figure 7.2. We see that the transfer functions $|H_1(f)|$ and $|H_2(f)|$ are peaking close to the cut-off frequency. This means that the voltages V_1 and V_2 at the OPAMPs outputs may drive the next stage into saturation. We can avoid this by equalizing the transfer functions so that all the maxima are equal to 0 dB . This can be done by increasing all the capacitances connected to the output of OPAMP AO1 (voltage V_1) by a scaling factor $k_1 = 1.300$. This will reduce the voltage V_1 while injecting the same amount of charges to the virtual ground to which the capacitances are connected to. We can do in a similar way for $|H_2(f)|$ by scaling all the capacitances connected to the output of OPAMP AO2 by a factor $k_2 = 2.279$. The resulting equalized transfer functions are plotted in Figure 7.7. We see that all the transfer functions have a maximum gain equal to 0 dB while the input-output transfer function remains unchanged.

7.1.2 ngspice

We can also check the equalized SC filter with ngspice using the same schematic as in Figure 7.4 with the scaled components. For this simulation ngspice had trouble to find the DC operating point with the 5th-order delay model. Reducing it to the 4th-order model solved the problem. The simulation result is compared to the theoretical transfer function in Figure 7.8. We see a perfect match despite the model for the delay had to be reduced to 4 instead of 5 for the other simulations.

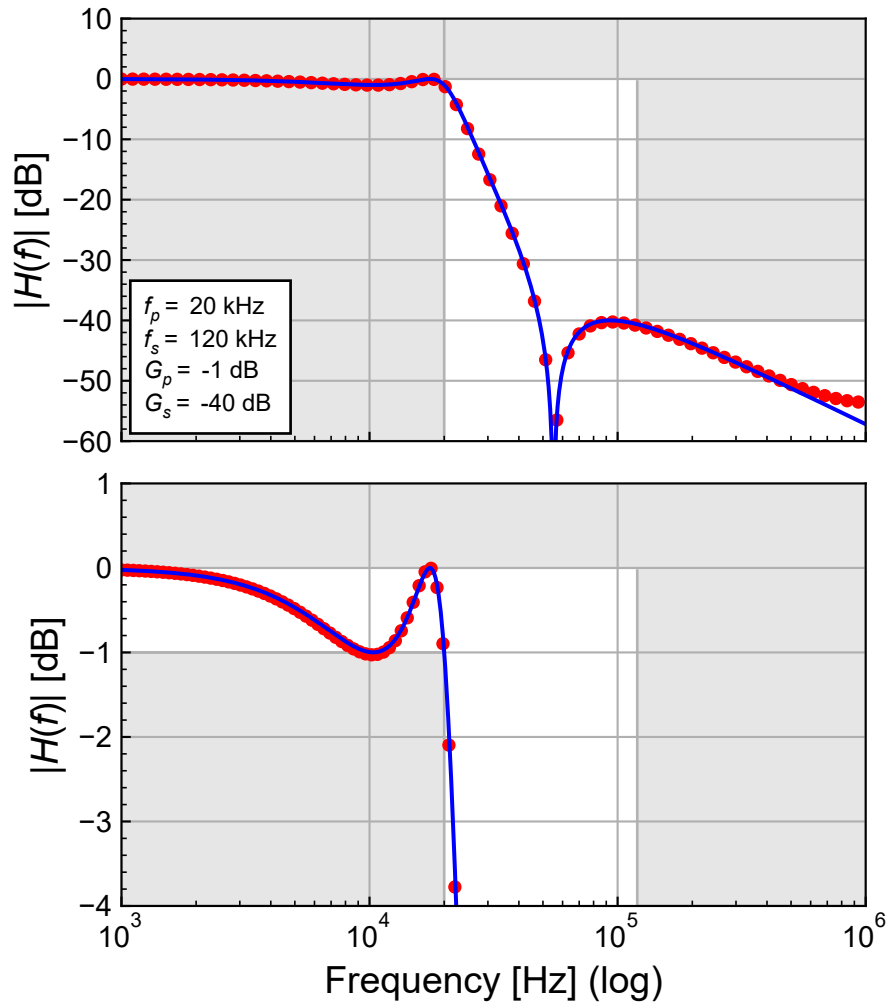


Figure 7.3: Theoretical transfer function magnitude of the 3rd-order active low-pass SC filter of Figure 6.1.

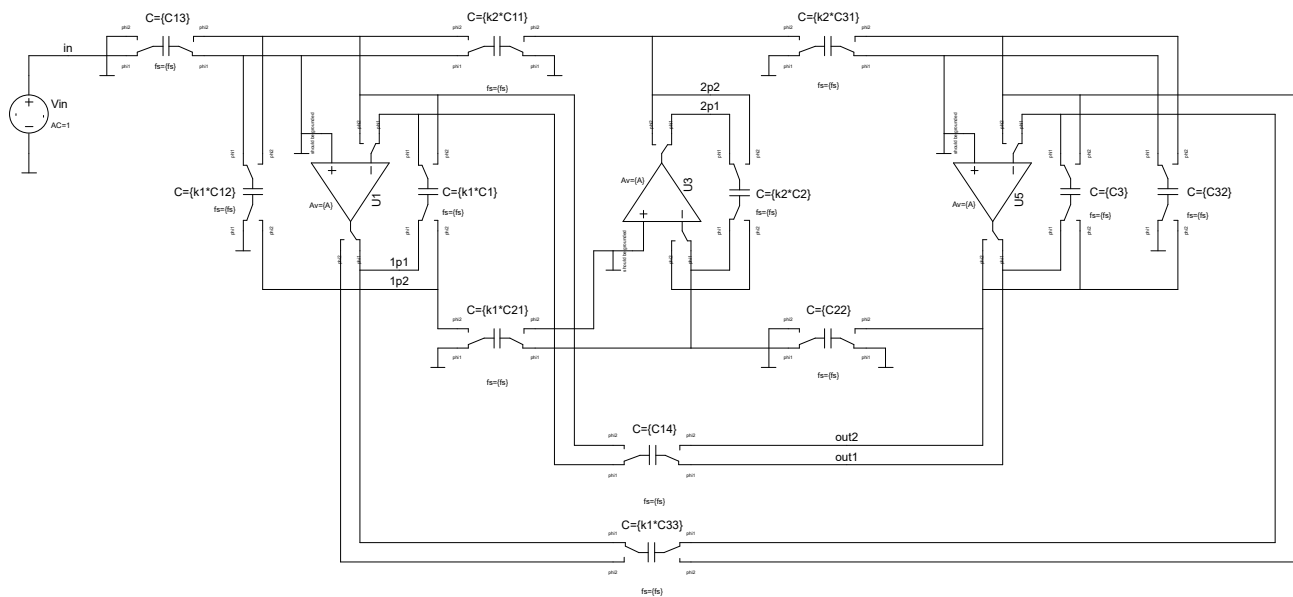


Figure 7.4: 3rd-order elliptic SC filter schematic used for LTSpice.

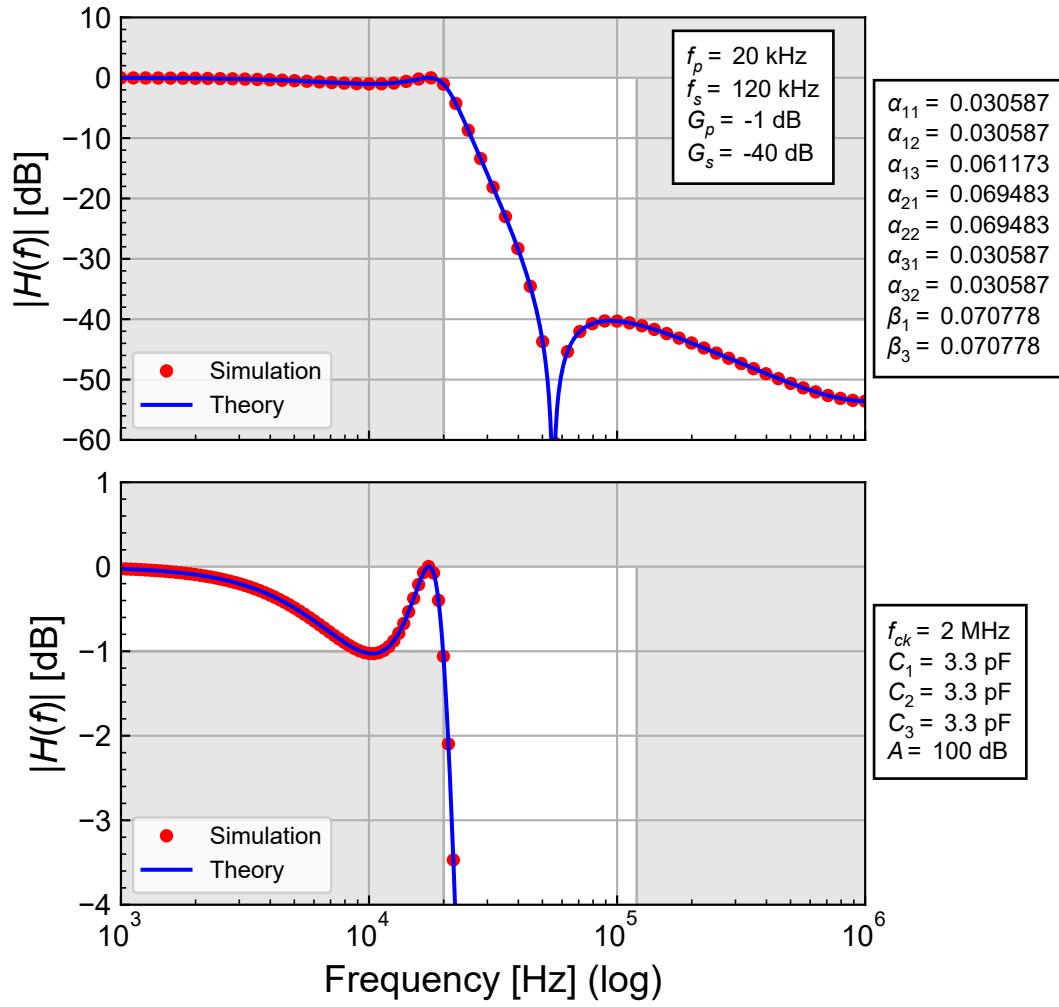


Figure 7.5: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

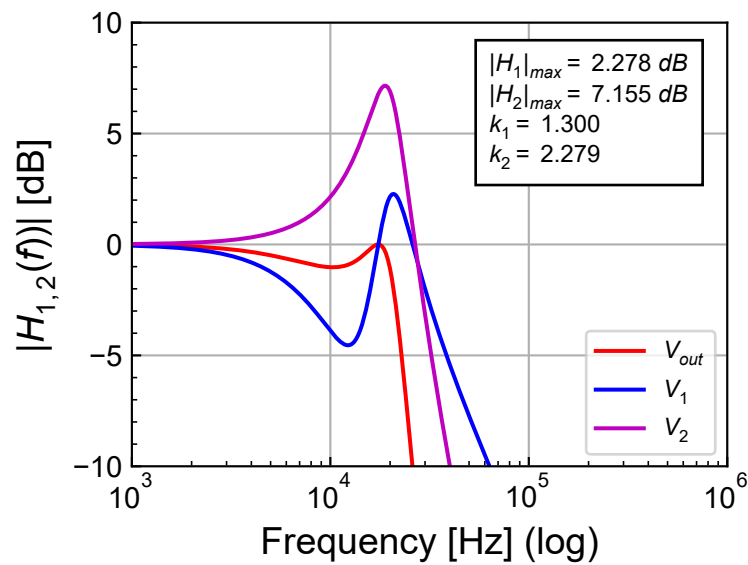


Figure 7.6: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

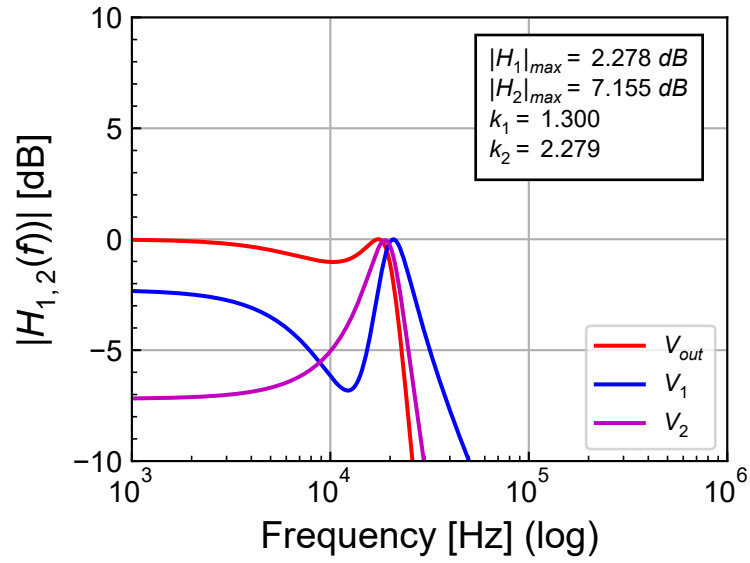


Figure 7.7: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

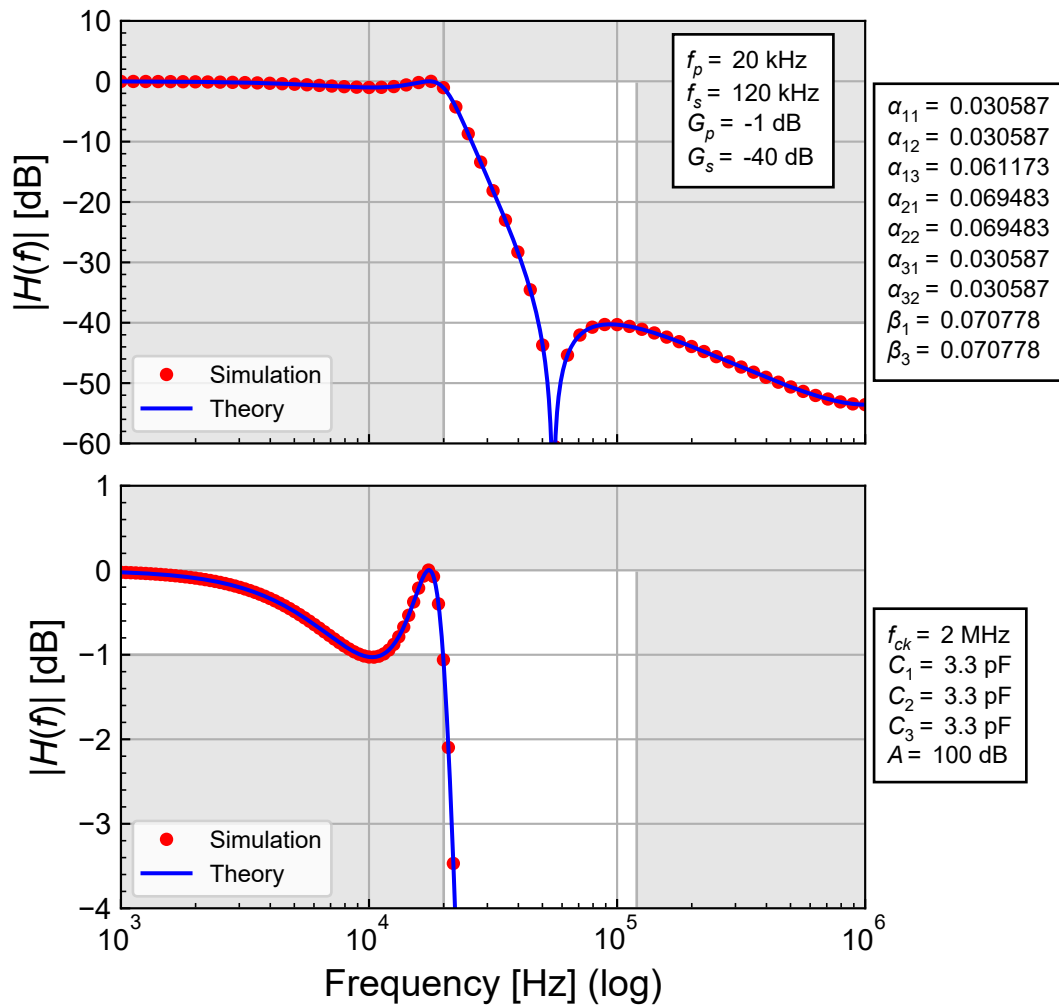


Figure 7.8: Simulated transfer function of the active 3rd-order low-pass SC filter of Figure 6.3.

8 Non-ideal effects

SC circuits are affected by many non-idealities coming from the OPAMP or OTA, the switches and the capacitances.

8.1 Switches

The non-idealities of the switches include:

- Finite on resistance of the MOS transistor(s),
- Resistance non linearity,
- Charge injection,
- Clock feedthrough and
- Noise.

None of these effects can be accounted for with the proposed AC simulation. The on resistance introduces a transient that may not reach steady-state.

8.2 OPAMP or OTA

The non-idealities of the OPAMP or OTA include:

- Finite DC gain,
- Finite gain-bandwidth product and
- Noise.

Since the proposed AC simulation assumes that the circuit has reached steady-state, the only non-ideality that can be simulated is the finite DC gain. We will simulate the 2nd-order low-pass filter with a very low gain but infinite bandwidth with the parameters given in Table 8.1.

Table 8.1: Component values of the 2nd-order active low-pass SC filter of Figure 5.4.

Symbol	Value	Unit
A	20	dB
f_{ck}	2	MHz
C_1	3.3	pF
C_2	3.3	pF
α_1	0.088857	-
α_2	0.044444	-
$C_{11} = \alpha_1 C_1$	293	fF
$C_{12} = \alpha_1 C_1$	293	fF
$C_2 = \alpha_2 C_2$	147	fF
$C_{21} = \alpha_2 C_2$	147	fF

The simulation result is compared to the ideal transfer function in Figure 8.1. We see that the DC gain has dropped by about 1 dB.

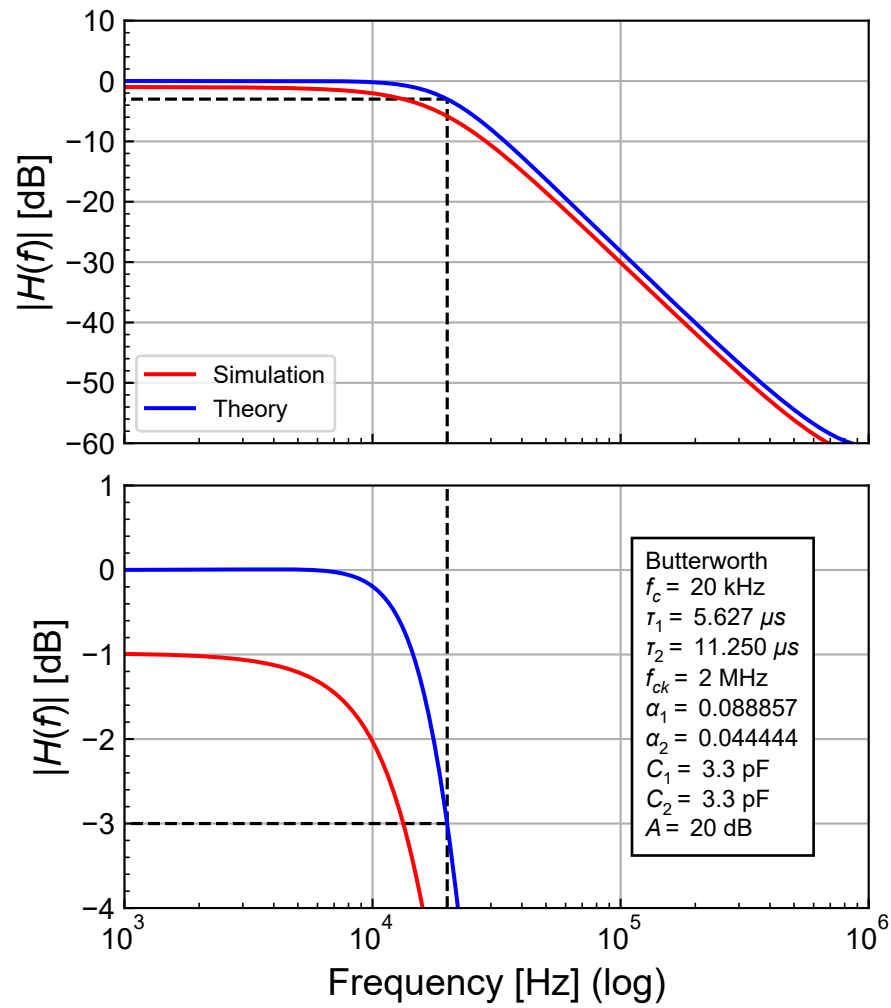


Figure 8.1: Simulated transfer function of the active 3rd-order low-pass SC filter of .

9 Conclusion

This notebook has presented a technique to simulate SC circuits such as filters using two non-overlapping phases using the AC simulation of a conventional Spice simulator such as LTSpice or ngspice. The circuits during phases Φ_1 and Φ_2 are described separately and run concurrently. They are then coupled by additional component in order to satisfy the charge conservation between phases. A special library has been developed for LTSpice (including the dedicated symbols) and ngspice to this purpose. Since the ideal time delay operator available in LTSpice does not exist in ngspice, an approximation of the ideal delay has been developed for ngspice using the XSpice `s_xfer` function.

This technique has then been illustrated with several examples starting with the simple passive 1st-order low-pass filter. Then a 1st-order active low-pass SC filter has been designed and simulated in LTSpice and ngspice. A 3rd-order active SC low-pass filter implementing a Chebyshev approximation has been designed and simulated with LTSpice and ngspice. Finally, a 3rd-order active SC low-pass filter implementing an elliptic approximation has been designed and simulated with LTSpice and ngspice. In this last example, the order for the time delay model had to be reduced from 5 to 4 in order for ngspice to find the correct DC operating point. All the simulated results agree perfectly with the theoretical transfer functions demonstrating the validity of the approach. It is important to recall that this approach is limited to AC simulations only.

Of course SC circuits can be simulated in more advanced simulators like Cadence Spectre, but this simple technique allows to quickly verify the design without the need to run a complex simulator.

References

- [1] Analog Devices, “LTSpice.” <https://www.analog.com/en/resources/design-tools-and-calculators/ltspace-simulator.html>, 2025.
- [2] Holger Vogt, Giles Atkinson, Paolo Nenzi, “Ngspice User’s Manual Version 43.” <https://ngspice.sourceforge.io/docs/ngspice-43-manual.pdf>, 2024.
- [3] D. Bielek, V. Biolkova, and Z. Kolka, “AC Analysis of Idealized Switched-Capacitor Circuits in Spice-Compatible Programs,” in *Proceedings of the 11th WSEAS international conference on circuits*, <https://www.wseas.us/e-library/conferences/2007csc/papers/561-533.pdf>, 2007, pp. 223–227.
- [4] D. Bielek, V. Biolkova, and Z. Kolka, “AC Analysis of Real Circuits with External Switching in PSpice,” in *Proceedings of the 12th WSEAS international conference on circuits*, <https://www.wseas.us/e-library/conferences/2007csc/papers/561-533.pdf>, 2008, pp. 193–196.
- [5] L. Pekar and E. Kureckova, “Rational Approximations for Time-Delay Systems: Case Studies,” in *Proceedings of the 13th WSEAS international conference on mathematical and computational methods in science and engineering*, https://www.researchgate.net/publication/262392699_Rational_approximations_for_time-delay_systems_case_studies, 2011, pp. 217–222.